

Digital Logic Practical Lab Report

Latches and Flip Flops

Student:

Abhiroop Mukherjee

Teacher:

Prof. Surajeet Ghosh

Prof. Sekhar Mandal

Course:

Digital Logic Laboratory (CS351)

EXPERIMENT 1 (a)


Objective

Design SR Latch using NAND gates to verify the state table of respective latches

Theory

An SR (Set/Reset) Latch works independently of control signal (like clock) and only relies on the state of S and R inputs.

 It can be made using two NAND gates as follows



where S' and R' are inverted inputs of S and R and Q and Q' are outputs.

- when $S = 1$ ($S' = 0$), we see that $Q = 1$, regardless of any value of Q' as $0 \cdot Q' = 0 = 1$
- when $R = 1$ ($R' = 0$), we see that $Q' = 1$, regardless of previous value of Q as $0 \cdot Q = 0 = 1$
- when $S = 0, R = 0$ ($S' = R' = 1$), the ~~values~~ output will either remains same, or will give $Q = Q' = 1$ (which is not good, and hence we call it "metastable" "latched")

d) when $S=1, R=1$ ($S'=R'=0$), the output will be $Q=Q'=1$, but that this output, will again get feeded to latch, and will continue to do so, into given sort of "infinite loop". This "metastable" is ~~unstable~~ condition, and should never be given as input,

→ From these observation, we get the following characteristic Table.

S'	R'	Q Q'
0	0	Meta stable
0	1	1
1	0	0
1	1	Latched.

Result

- Avoiding "Latched" and "Metastable" conditions, the output of the simulator made circuit matches with the Characteristic Table
- Two NAND gates were used to make the SR Latch

Inputs / Outputs:

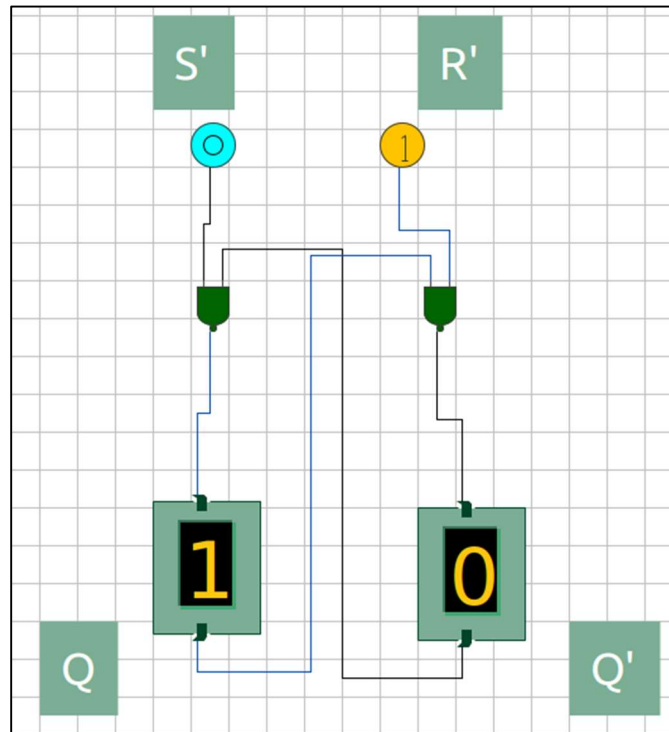


Figure 1: $S' = 0$, $R' = 1$; $Q = 1$, $Q' = 0$

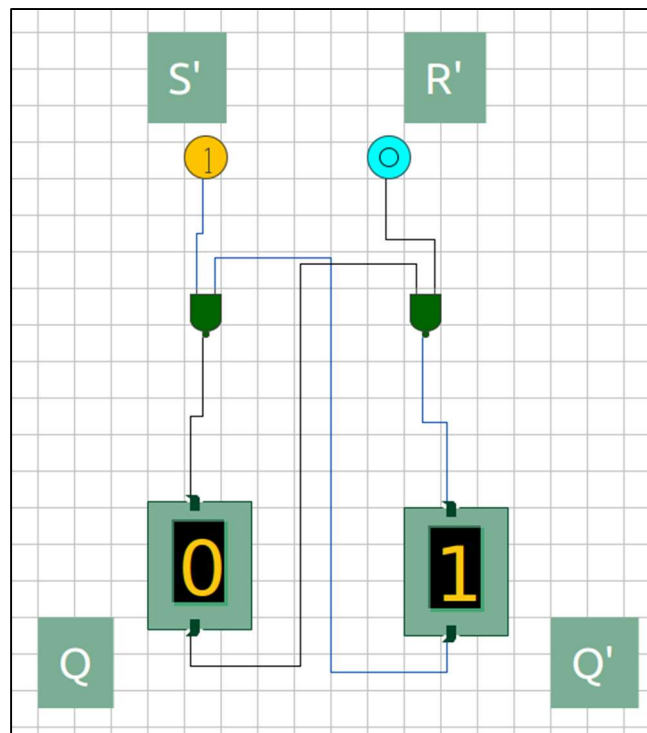


Figure 2: $S' = 1$, $R' = 0$; $Q = 0$, $Q' = 1$

EXPERIMENT 1 (b)

Objective


Design D Latch using NAND gates to verify the state table of respective Latch.

Theory

- The D Latch is used to store, or capture the logic level which is present data line.
- It's Characteristic Table is as follows.

D	Q	Q'
0	0	1
1	1	0

 - We can use three NAND gates to develop the D Latch.



Result

- Three NAND gates were used to design D Latch
- The output from the simulator matches with the Characteristic Table.

Inputs / Outputs:

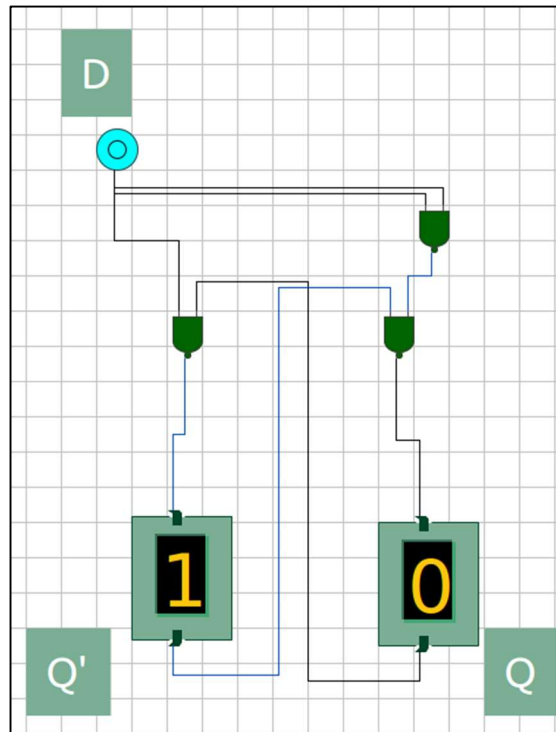


Figure 2: $D = 0$; $Q = 1$, $Q' = 0$

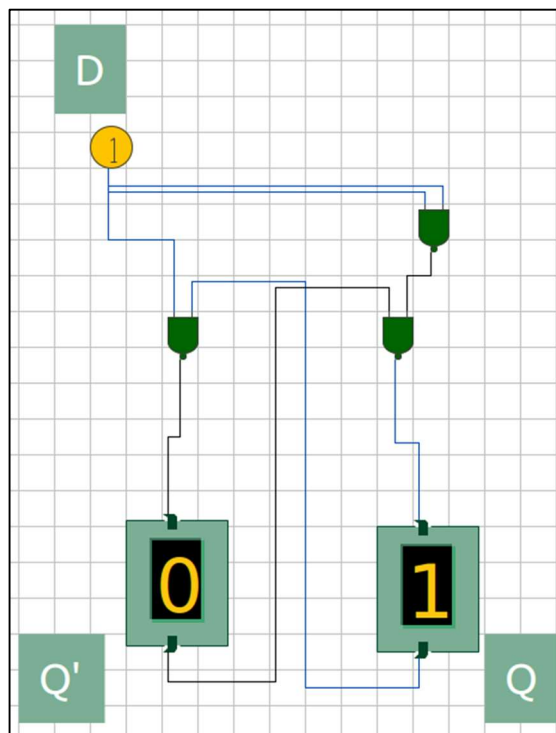


Figure 2: $D = 1$; $Q = 0$, $Q' = 1$


EXPERIMENT 2 (b)

Objective

Verify the Truth Table of a J-K Master Slave Flip-Flop.

Theory

Given Circuit is as follows:

 

It's Characteristic Table is as follows:

$Q(t)$	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

→ as it's not possible to display both previous $Q(t)$ and present $Q(t+1)$ simultaneously, ~~we can't~~ we will only see the present $Q(t+1)$ outputs.

→ also as we are using NAND gates, clear will be set to 1 always during operation as $\overline{1 \cdot x} = \overline{x}$

Result

→ The output of the simulator matches with the Characteristic Table

→ It is to be noted that as we are using Master Slave JK Flip Flop, we get output after two clock cycles, instead of one.

Inputs / Outputs:

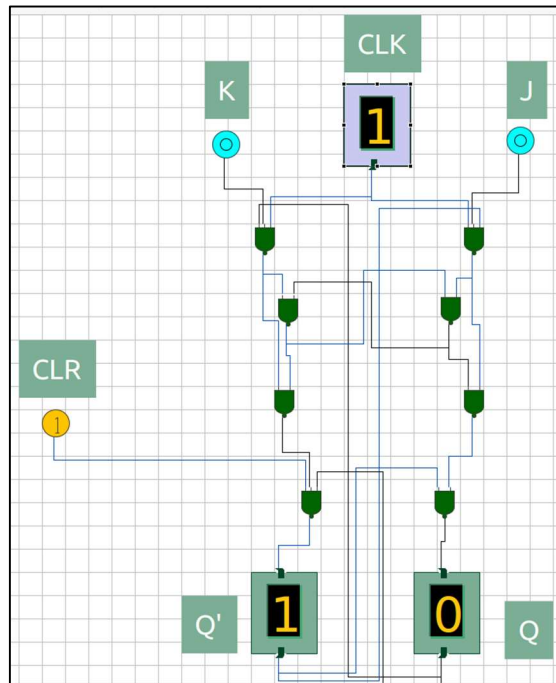


Figure 3: $Q(t) = 0, J = 0, K = 0; Q(t+1) = 0$

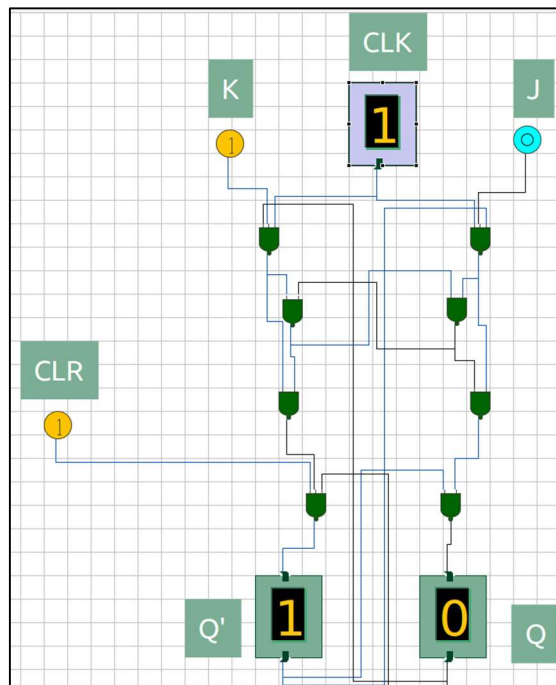


Figure 2: $Q(t) = 0, J = 0, K = 1; Q(t+1) = 0$

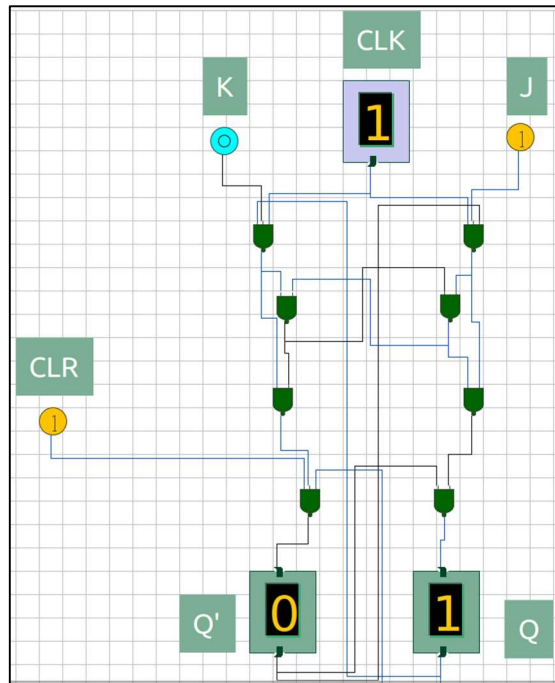


Figure 3: $Q(t) = 0, J = 1, K = 0; Q(t+1) = 1$

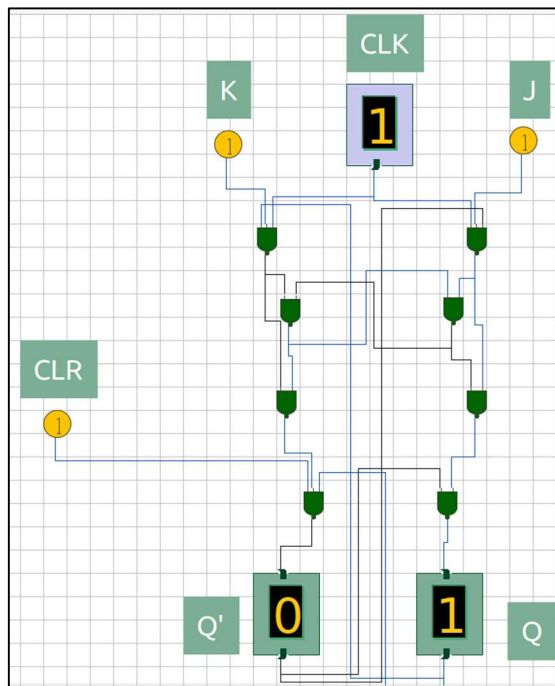


Figure 4: $Q(t) = 0, J = 1, K = 1; Q(t+1) = 1$

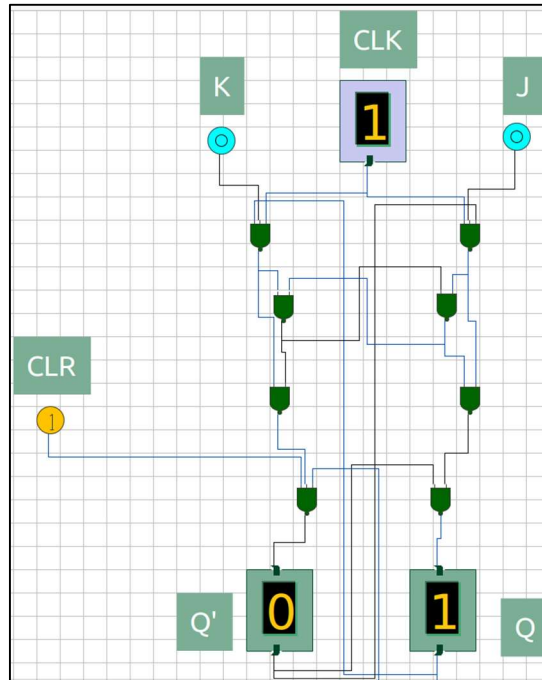


Figure 5: $Q(t) = 1, J = 0, K = 0; Q(t+1) = 1$

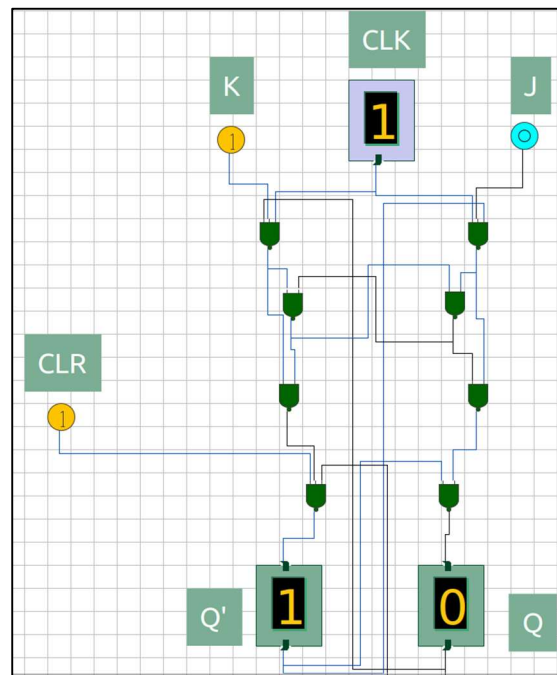


Figure 6: $Q(t) = 1, J = 0, K = 1; Q(t+1) = 0$

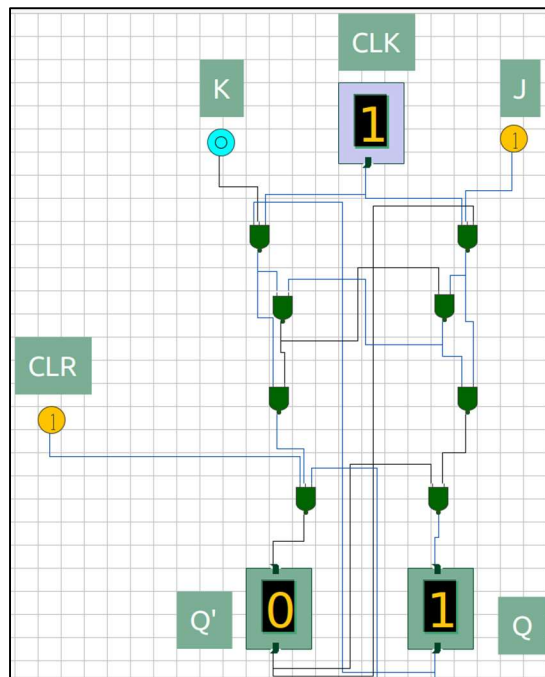


Figure 7: $Q(t) = 1, J = 1, K = 0; Q(t+1) = 1$

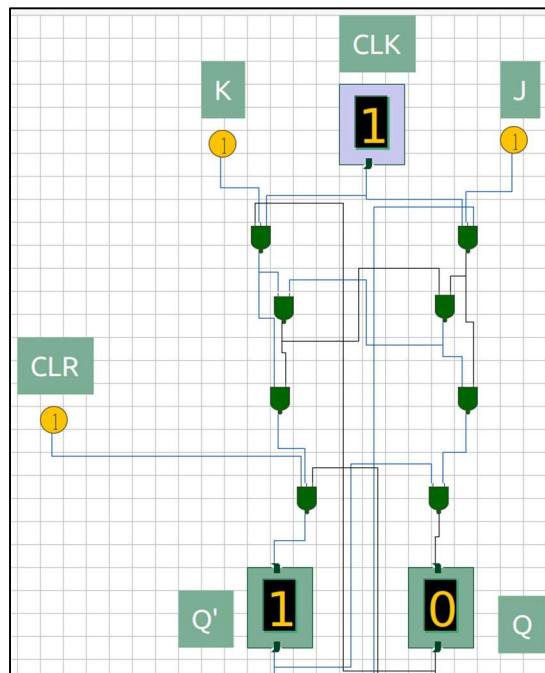


Figure 8: $Q(t) = 1, J = 1, K = 1; Q(t+1) = 0$

EXPERIMENT 2 (b)

Objective

Realise a D Flip Flop and verify the state table


Theory

→ The D (Delay) Flip-Flop is a modified version of S-R Flip-Flop with addition of an inverter to prevent the S and R inputs from being at the same Logic Level

→ It's Characteristic Table is as follows:

$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

 → We can realise following D Flip-Flop Circuit



Result

→ We have used five NAND gates to realize D Flip-Flop.

D Flip-Flop

→ The output of simulator matches with the characteristic Table.

Inputs / Outputs:

 


Figure 4: $Q(t) = 0$, $D = 0$; $Q(t+1) = 0$

 


Figure 2: $Q(t) = 0$, $D = 1$; $Q(t+1) = 1$

 


Figure 3: $Q(t) = 1, D = 0; Q(t+1) = 0$

 


Figure 4: $Q(t) = 1, D = 1; Q(t+1) = 1$

EXPERIMENT 2 (c)

Objective

Design an Edge-Triggered D Flip-Flop and verify state Table

Theory

→ Edge-Trigger is a property of Flip-Flop which defines when output is ~~also~~ displayed

→ a clock input in Sequential Looks like the fall




→ an ~~out~~ response to input can be displayed at two timings according to clock

i) When Clock goes from 0 to 1

ii) when clock goes from 1 to 0

→ These two ~~big~~ trigger timing as described as positive edge-trigger and negative edge trigger respectively.

→ Following ~~graph~~ circuit was given:

 

→ And the characteristic Table of D Flip Flop is as follows

$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

→ As we are using NAND gates, Clear and preset should be kept 1 as $\overline{1 \cdot x} = \overline{x}$

→ As multiple Latches (depth = 2) are being used in the circuit, the output requires multiple clock pulses (2) to display as output.

Result

→ The outputs from the simulator is same as what we expected from the characteristic Table.

Inputs / Outputs:

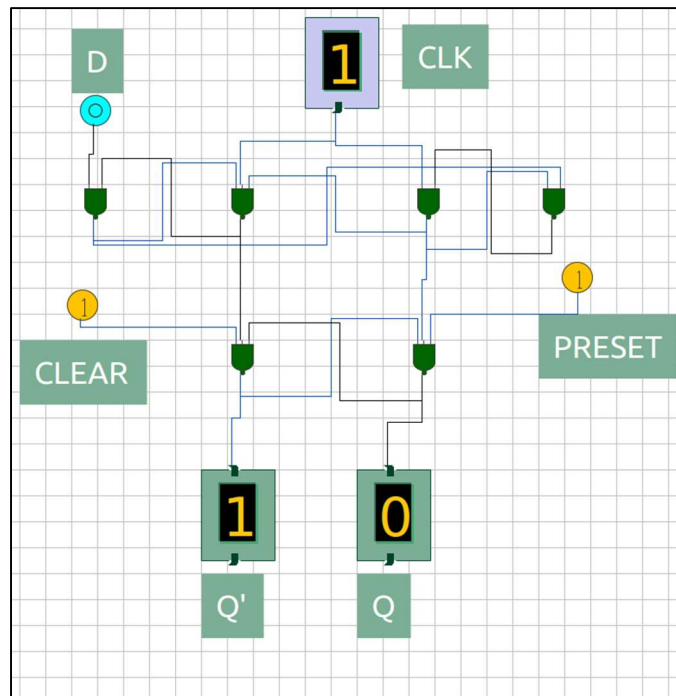


Figure 5: $Q(t) = 0$, $D = 0$; $Q(t+1) = 0$

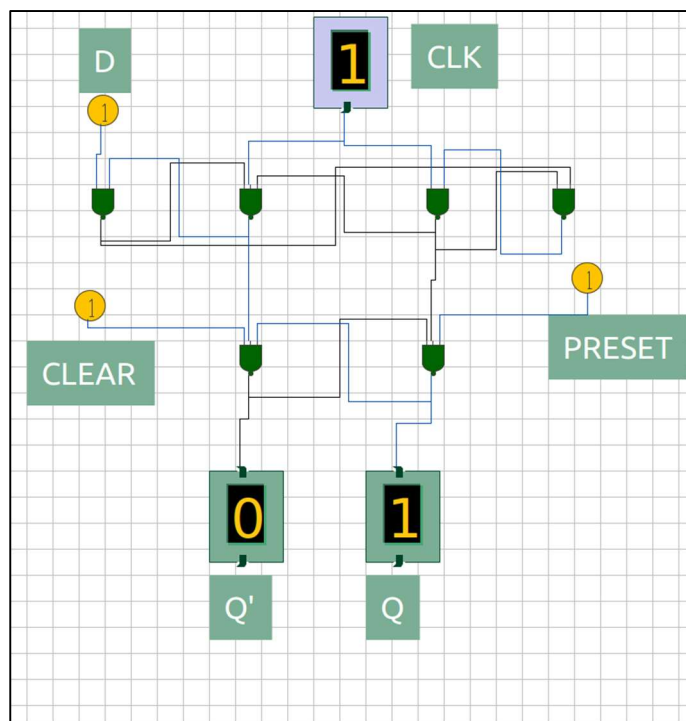


Figure 2: $Q(t) = 0$, $D = 1$; $Q(t+1) = 1$

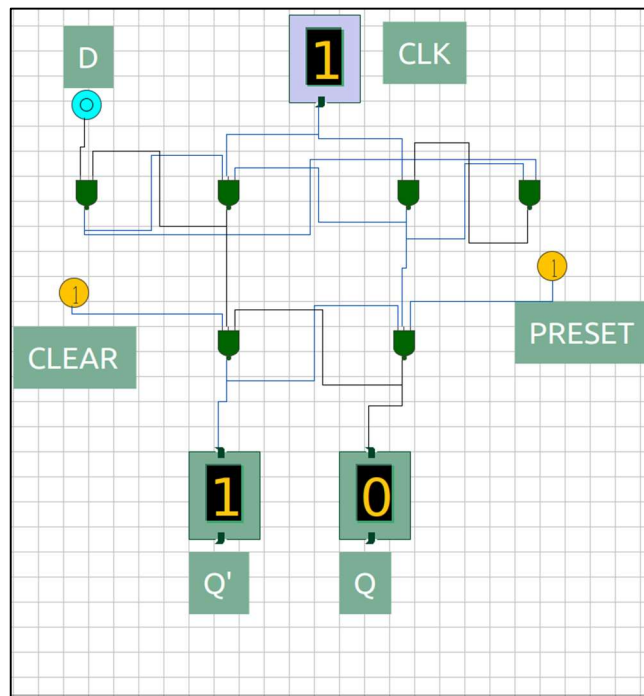


Figure 3: $Q(t) = 1, D = 0; Q(t+1) = 0$

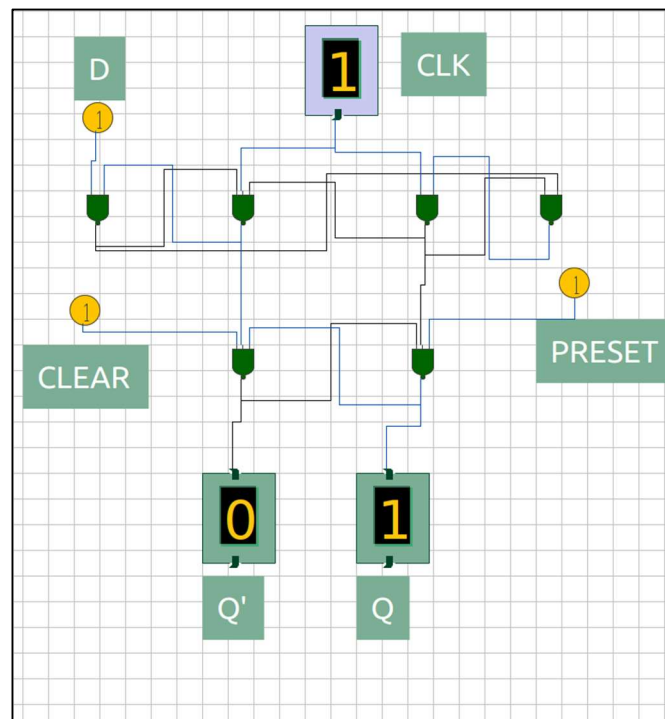


Figure 4: $Q(t) = 1, D = 1; Q(t+1) = 1$