 


# Digital Logic Laboratory

## Assignment No. 4

### Objective:

1. Design SR and D latches using NAND gates to verify the state table of respective latches.
2. Build flip-flops using NAND gates to:
  - a) verify the truth-table of a J-K Master Slave Flip-flop.



- b) realise a D Flip-flop and verify the state table.
- c) design an edge-triggered D Flip-flop and verify the state table.

