

5/17

Indian Institute of Engineering Science and Technology, Shibpur  
Five year Dual Degree (B.Tech-M.Tech) 3<sup>rd</sup> Semester



Examination <Year>  
<Digital logic> <CS 301>

Full marks: 70



Time: 3 hours

(Answer any five)

 
 
1. (a) Realize NAND gate using NOR gate.
- (b) Prove that the following circuit (Fig.1) is same as NOT i.e. negation of a Boolean variable A.



  - (c) Prove that  $A[AB+C(D'+A)+B] = AB+AC$
- (d) Find Dual of  $x+x'y = x+y$
- (e) Prove that  $AB+ABC+ABCD+ABCDE+ABCDEF = AB$
- (f) A Boolean function  $Q(x, y)$  is implemented using a 2x4 decoder (Fig.2). What is  $Q(x, y)$ ?
- (g) Find  $Z(A, B, C)$ , the output of Fig.3.
- (h) Draw Karnaugh map for  $F(A, B, C) = A'+B+C$
2. (a) How many adjacent cells in a Karnaugh map must be circled to eliminate 3 variables? [2+2+2+1+1+2+2+2]
- (b) Simplify  $F(A, B, C, D) = \sum (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$  using Karnaugh map and find the number of literals in the simplified equation of F.
- (c) What is hazard? How hazard can be avoided?
- (d) How many clock pulses are counted by n-bit Ring and Johnson counter?
- (e) Find  $F(P, Q, R)$  in simplified form (Fig.4). [1+4+(1+3)+2+3]



  3. (a) In the sequential circuit shown in Fig. 5 below the initial output  $Q_1Q_0$  is 00. What are the values of  $Q_1Q_0$  at the consecutive four clock pulses?



- (b) Find F in simplified form (Fig.6).
- (c) Express the Boolean function  $F=xy+x'z$  in POS form.
- (d) Draw the OR-AND circuit of the simplified Boolean function  $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$  assuming that the complement inputs are available. [4+4+2+4]
4. (a) Obtain 9's and 10's complement of the following decimal numbers.

- (i) 13579 (ii) 09900 (iii) 90090
- (b) Perform the following subtraction using 9's complement  
 (i) 5250-321 (ii) 753-864 (iii) 20-1000 (iv) 1753-8640 [6+8]
5. (a) Design the binary synchronous counter having the following repeated binary sequence using T flip flops. (i) 0, 1, 2, 0 (ii) 0, 3, 2, 0
- (b) Draw and explain the operation of NAND and NOR gate using CMOS. [8+6]
6. (a) Design a clocked sequential circuit whose state diagram is given in **Fig.7** using T flip flop.
- (b) How many clock pulses are required to shift 8 bit data through a 4-bit shift register and why?
- (c) Draw the circuit of a Mod-10 ripple counter using negative edge triggered J-K flip flop. Find the repetition rate of this counter when the clock time is  $T_c$ . [6+2+4+2]
7. (a) Compare the performance of DTL, TTL, CMOS logic on the basis of power dissipation and propagation delay.
- (b) Find the fan out of a RTL gate for  $I_{Csat}=5.31$  mA and  $h_{FE}>7$ .
- (c) What is the propagation delay time of open collector TTL, totem pole TTL and schottky TTL? [6+5+3]

