

INDIAN INSTITUTE OF ENGINEERING SCIENCE AND TECHNOLOGY, SHIBPUR

B.E. 3rd SEMESTER (CS) MID TERMINAL EXAMINATION, 2016

Digital logic (CS301)

FULL MARKS: 50

TIME: 2 Hrs

1. (a) Simplify the following Boolean expressions to a minimum number of literals.
(i) $ABC + A'B + ABC'$ (ii) $(BC' + A'D)(AB' + CD')$
(b) Reduce the followings
(i) $A'C' + ABC + AC'$ to three literals
(ii) $(A' + C)(A' + C')(A + B + C'D)$ to four literals [4+6]
2. (a) Find the complement of (i) $(AB' + C)D' + E$ (ii) $(X + Y' + Z)(X' + Z')(X + Y)$
(b) Simplify $F = XY'Z + X'Y'Z + W'XY + WX'Y + WXY$ using K-map. Realize the simplified logic function using two input NAND gate. [4+6]
3. (a) Find the essential prime implicants of the function
 $F(W, X, Y, Z) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$
(b) Simplify F together with the don't care condition. Realize the simplified expression using two NOR gates assuming that all the normal and complement inputs are available.
 $F(A, B, C, D) = \sum(0, 1, 2, 9, 11)$, $d(A, B, C, D) = \sum(8, 10, 14, 15)$
(c) A logic circuit has 4 inputs and 1 output. The output is equal to 1 when all the inputs are 1 or none of the inputs are equal to 1 or an odd number of inputs are 1. Find the simplified output function in SOP. [2+5+3]
4. (a) Design one full adder using two half adder and one OR gate.
(b) Design full adder using two 4:1 MUX.
(c) Discuss about the advantages and disadvantages of ripple carry adder and carry look ahead adder? [2+4+4]
5. (a) Draw the circuit and explain the operation of CMOS inverter.
(b) In a DTL circuit voltage across conducting diode is 0.7 volt, cut in voltage of the diode is 0.6 volt, cut in voltage of the transistor is 0.5 volt, $V_{CEsat} = 0.2$ volt, $V_{BEsat} = 0.8$ volt, $\beta = 30$. Find the logic 0 and logic 1 noise margin. [4+4+2]
(c) Draw Venn diagram illustration of $X.(Y+Z)$.


FULL MARKS: 70

TIME: 3 Hrs

(Answer any five)

1. (a) Find the 9's complement of the following 8-digit decimal numbers.
(i) 12349876 (ii) 00980100 (iii) 90009951 (iv) 67543218
- (b) Perform subtraction with the following unsigned decimal numbers by taking the 10's complement of the subtrahend.
(i) 5250-1321 (ii) 1753-8640 (iii) 20-100 (iv) 1200-250
- (c) In a DTL circuit voltage across conducting diode is 0.7 volt, cut in voltage of the diode is 0.6 volt, cut in voltage of the transistor is 0.5 volt, $V_{CEsat}=0.2$ volt, $V_{BEsat}=0.8$ volt, $\beta=30$. Find the logic 0 and logic 1 noise margin.
- (d) The state of a 12-bit register is 010110010111. What is the content of the register in BCD and in excess-3 code? [2+6+4+2]

 2. (a) Prove that $xy+x'z+yz=xy+x'z$
- (b) Simplify the following Boolean expressions to a minimum number of literals.
(i) $x'yz+xz$ (ii) $xy+x(wz+wz')$
- (c) Find the complement of $F = x+yz$. Show that $F.F'=0$ and $F+F'=1$.
- (d) Convert the following expressions into SOP and POS.
(i) $(AB+C)(B+C'D)$ (ii) $x'+x(x+y')(y+z')$
- (e) Show that dual of Exclusive-OR is its complement. [1+3+4+4+2]



3. (a) Simplify the following Boolean function using K-map.
(i) $F(A, B, C, D) = \prod(0, 1, 2, 3, 4, 10, 11)$
- (b) Find the essential prime implicants of the following Boolean function.
 $F(W, X, Y, Z) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$
- (c) Simplify F together with the don't care condition.
 $F(A, B, C, D) = \sum(0, 1, 2, 9, 11)$, $d(A, B, C, D) = \sum(8, 10, 14, 15)$
- (d) Simplify the following Boolean functions using K-map and implement them using 3-level NOR gate.
(i) $F(W, X, Y, Z) = WX' + Y'Z' + W'YZ'$ (ii) $F(W, X, Y, Z) = \sum(5, 6, 9, 10)$ [2+2+3+7]

4. (a) Design a combinational circuit with three inputs (A, B, C) and one output (Y). The output is equal to 1 when the binary value of the input is less than 3. Otherwise the output is 0.
- (b) Design a combinational circuit that adds one to a 4-bit binary number ($A_3A_2A_1A_0$) using four half adders.
- (c) Prove the followings:
(i) $x' \oplus y = x \oplus y' = (x \oplus y)'$ (ii) $x \oplus 1 = x'$ and $x \oplus 0 = x$ (iii) $x \oplus y = x + y$ if $xy = 0$
- (d) Define the following terms.
(i) Fan out (ii) Propagation delay (iii) Noise margin [2+2+2+1+1+6]

5. (a) Implement the following Boolean function using 8x1 MUX.
 $F(A, B, C, D) = \sum(0, 3, 5, 6, 8, 9, 14, 15)$
- (b) Draw the block diagram of a 5x32 decoder using four 3x8 decoders with enable input and one 2x4 decoder.
- (c) Design a combinational circuit that compares two 4-bit numbers A and B to check if they are equal. The output of the circuit (X) is 1 if $A=B$ and 0 if $A \neq B$.
- (d) Draw and explain the operation of a CMOS NAND. [4+5+2+3]

(7-1)

$$A + B + C' + D$$

$$(\overline{x} + y)(x + \overline{y}) = x + y$$

OH
1H
1L
0L





Design a circuit of a 4-bit binary up ripple counter using negative edge triggered J-K flip flop.

(b) A flip flop has 10 ns propagation delay. What is the maximum delay of a 10-bit binary ripple counter and synchronous counter using such flip flops?

(c) How many clock pulses are required to shift 8-bit data through a 4-bit shift register?

  (d) Write the output of the circuit in figure 1 for six clock pulses. Assume that the initial value of Q is 0.



(e) Design a clocked sequential circuit whose state diagram is shown in figure 2. Design the circuit using J-K flip flop. [3+2+1+2+6]

(a) What is the content of the shift register in figure 3 after 3 clock pulses? Assume that the initial content of the register is 0110.

(b) The characteristic table of X-Y flip flop is given below. Implement it using J-K flip flop.



X	Y	Q_{n+1}
0	0	1
0	1	Q_n
1	0	Q_n'
1	1	0

(c) What is the mod value of an n-bit ring counter and switch-tail counter?

(d) Draw the block diagram of a 16x4 RAM. Explain the read and write operation.

(e) Find the mod value of the counter in figure 4.

[3+2+2+4+3]

  


$$xy + x'z + yz = xy + x'z$$

$$xy + x'z + yz(x + x')$$

$$= xy + x'z + xyz + x'y z$$

$$= xy(1+z) + x'z(1+y)$$

$$= xy + x'z$$

 

$$0011 \quad 0011$$

$$= 4 \times (2-1)$$

$$= 4$$

$$x + (6-1)$$

$$= x + 5$$

$$1010 \quad 0100 \quad 0001 \quad 1000$$