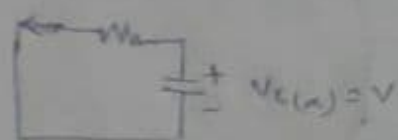


The switch is closed at position 1 for a long time. At $t=0$ it moves to position 2. Find $i(t)$.

At $t=0^-$ $V_C(0^-) = V = \text{supply voltage}$



KVL at $t=0^+$ $R i(t) + \frac{1}{C} \int_0^t i(t) \cdot dt + V_C(0^+) = 0$

$$R i(t) + \frac{1}{C} \int_0^t i(t) \cdot dt = -V_C(0^+)$$

$$\frac{R di(t)}{dt} + \frac{1}{C} \cdot i(t) = 0$$

$$\frac{di(t)}{dt} + \frac{1}{RC} \cdot i(t) = 0$$

$$i(t) = K e^{-\frac{1}{RC} t}$$

at $t=0^+$ $V_C(0^+) = -V$

$$i(0^+) = -\frac{V}{R}$$

$$-\frac{V}{R} = K e^{-\frac{1}{RC} \times 0}$$

$$K = -\frac{V}{R}$$



$$i(t) = -\frac{V}{R} e^{-\frac{1}{RC} t}$$

$$V_R(t) = R \cdot i(t) = -V \cdot e^{-\frac{1}{RC} t}$$

$$V_R(t) + V_C(t) = 0$$


$$V_C(t) = -V_R(t)$$

$$V_C(t) = V e^{-\frac{t}{RC}}$$

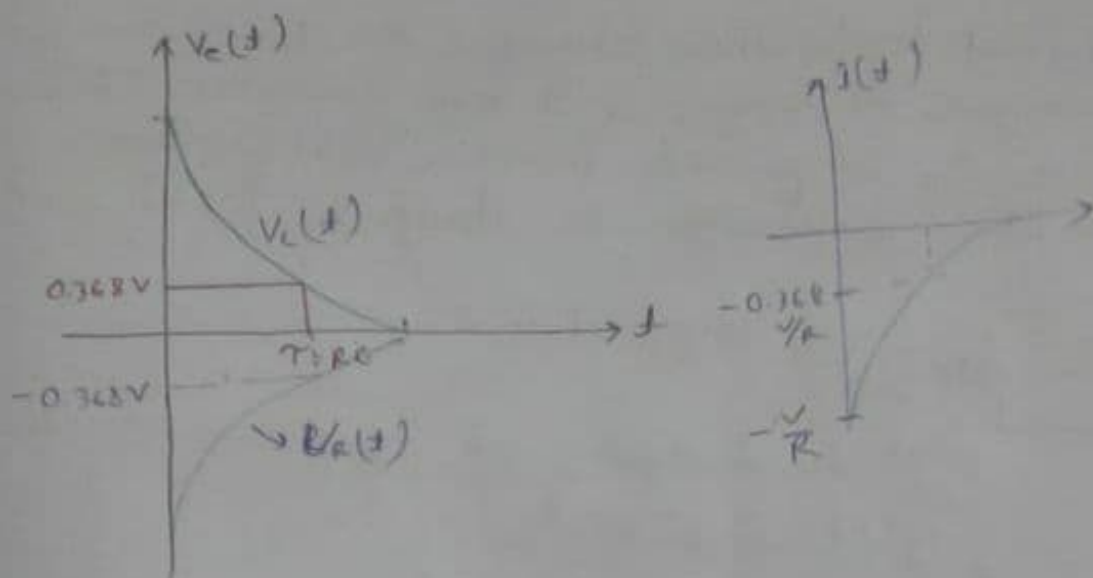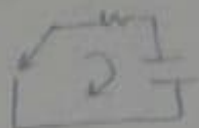

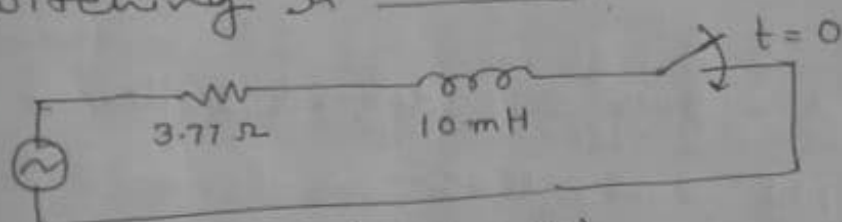Q.1) Grade - 2019

In the circuit shown below, the switch is closed at $t=0$, the value of θ in degrees which will give the maximum value of DC offset of the current at the time of switching is _____?



$$v(t) = 150 \sin(377t + \theta)$$

$$i(t) = \underbrace{k e^{-\frac{R}{L}t}}_{\text{DC offset part}} + \frac{V_m}{Z} \sin(\omega t + \phi) - \tan^{-1} \frac{\omega L}{R}$$

$$k = -\frac{V_m}{Z} \sin\left(\phi - \tan^{-1} \frac{\omega L}{R}\right)$$




at $t=0$ DC offset value is maximum.

$$\text{so, } -(\theta - \tan^{-1} \frac{\omega L}{R}) = 90^\circ$$

$$\theta - \tan^{-1} \frac{377 \times 10 \times 10^{-3}}{3.77} = -90^\circ$$


$$\theta - 45^\circ = -90^\circ$$

$$\boxed{\theta = -45^\circ}$$

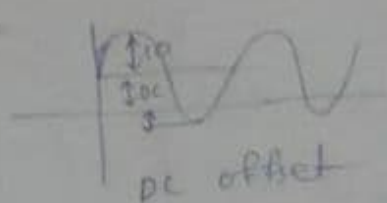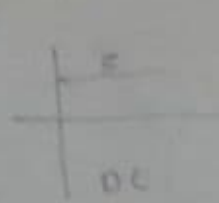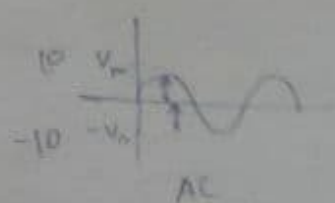

P.2 *gate-2008*

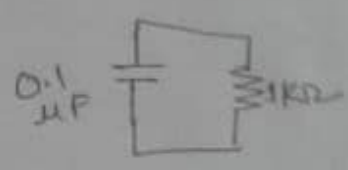A $0.1 \mu\text{F}$ capacitor charged to 100 V is discharged through a $1 \text{ K}\Omega$ resistor. The time in ms required for the voltage across the capacitor to drop to 1 V is —?



$$V_c(0) = 100 \text{ V}$$

discharging of capacitor equation

$$V_c(t) = V_c e^{-t/\tau}$$

$$\tau = RC = 10^3 \times 0.1 \times 10^{-6} \times 10^{-3}$$

$$= 10^{-4} \text{ sec}$$

$$V_c(t) = 100 e^{-10^4 t}$$

$$1 = 100 e^{-10^4 t}$$

$$t = 0.46 \text{ msec}$$

P.3 *gate-2013*

Consider the two CTS defined below


$$x_1(t) = \begin{cases} |t| & -1 \leq t \leq 0 \\ 0 & \text{otherwise} \end{cases}$$

$$x_2(t) = \begin{cases} 1 - |t| & -1 \leq t \leq 0 \\ 0 & \text{otherwise} \end{cases}$$



These signals are sampled with a sampling period of $T = 0.25 \text{ sec}$ to obtain discrete time signals $x_1[n]$ and $x_2[n]$ respectively.

which one of the following statements are true?

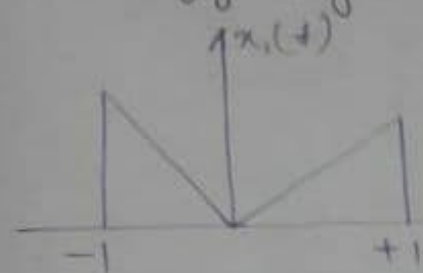
- Ⓐ Energy of $x_1[n] >$ Energy of $x_2[n]$
- Ⓑ Energy of $x_2[n] >$ Energy of $x_1[n]$
- Ⓒ $x_1[n]$ & $x_2[n]$ have eq energy
- Ⓓ Neither $x_1[n]$ nor $x_2[n]$ is a finite energy signals.



$T_s = 0.25$
Sampling

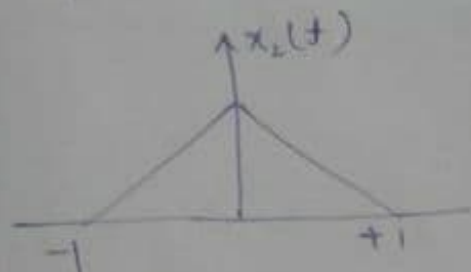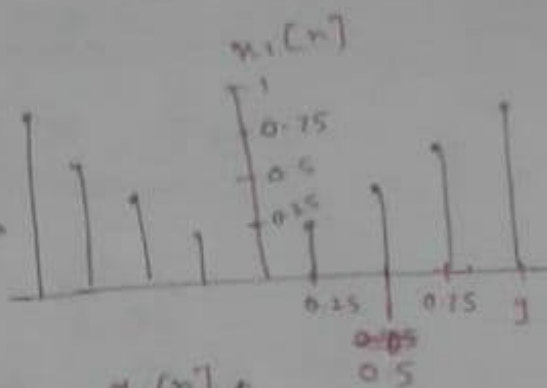


$T_s = 0.25$

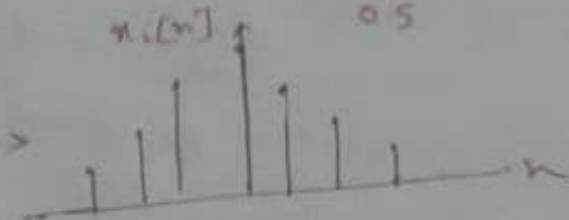

$$E_1 = \sum_{n=-\infty}^{\infty} |x_1[n]|^2 = 0^2 + 2[1^2 + 0.75^2 + 0.5^2 + 0.25^2]$$

$$E_2 = \sum_{n=-\infty}^{\infty} |x_2[n]|^2 = 1^2 + 2[0.75^2 + 0.5^2 + 0.25^2 + 0^2]$$

$$E_1 > E_2$$

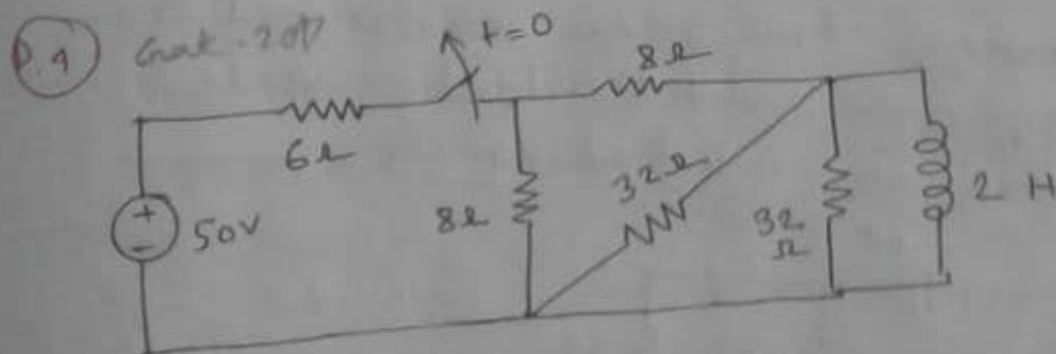

the switch in the fig was closed for a long time, It is opened at $t=0$, the current in the inductor of 2H for $t \geq 0$ is _____


at $t = 0^-$



$$I = 5A$$

$$I_L = \frac{5}{2} = 2.5A$$

at $t = 0^+$

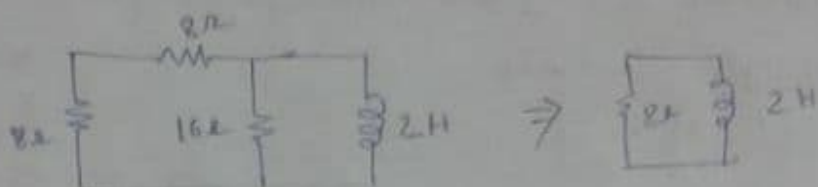

$$2 \frac{di(t)}{dt} + 8i(t) = 0$$

$$\frac{di(t)}{dt} + 4i(t) = 0$$

$$i(t) = K e^{-4t}$$


at $t = 0^+$ $i_L(0^-) = i_L(0^+) = 2.5$


$$K = 2.5$$

$$i(t) = 2.5 e^{-4t}$$

(P5) gate-2017

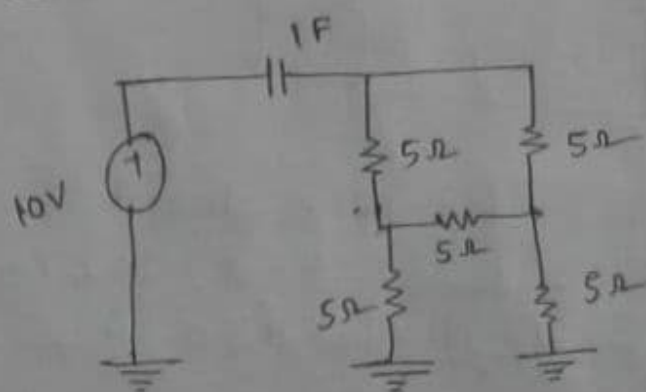The initial charge in the $1F$ capacitor present in the circuit shown is zero. The energy in joules transformed from the DC source until steady state condition is reached equals _____.



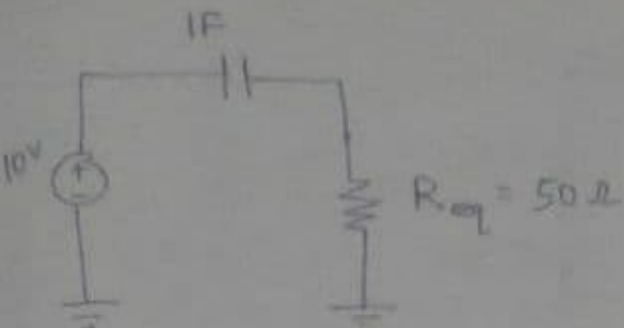

at $t = 0^-$, $v_c(0^-) = 0$

Final voltage $v_c(t) = 0$

$$R_{eq} i(t) + \frac{1}{C} \int_0^t i(t) \cdot dt = 10$$

$$\frac{di(t)}{dt} + \frac{1}{R_{eq} C} i(t) = 0$$

$$\frac{di(t)}{dt} + \frac{1}{5} i(t) = 0$$

$$i(t) = K \cdot e^{-\frac{1}{5}t}$$

at $t = 0^+$ $i(0^+) = \frac{10}{5} = 2A$

$$K = 2$$

$$i(t) = 2 e^{-t/5}$$


instantaneous power, $p = V \times i_r$
 $= 10 \times 2 \cdot e^{-t/5}$
 $= 20 \cdot e^{-t/5}$

Energy transferred $= \int_0^{\infty} p dt = \int_0^{\infty} 20 \cdot e^{-t/5} dt$
 $= 100 J$



(P.6) gate-2016

In the ckt pr shown, switch S_2 has been closed for a long time, at time $t = 0$, switch S_1 is closed.

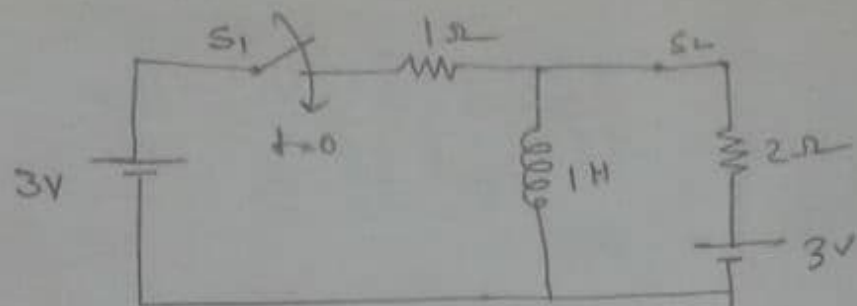At $t = 0^+$, the rate of change of current through the inductor in ampere/sec is -?



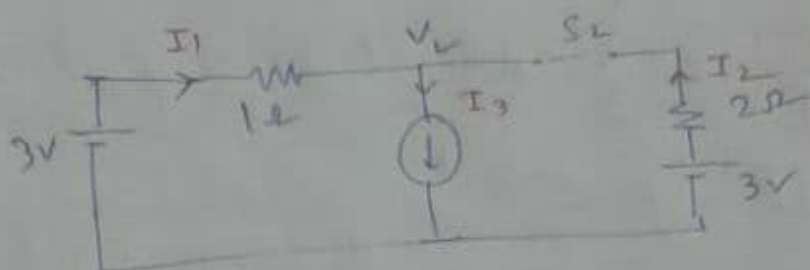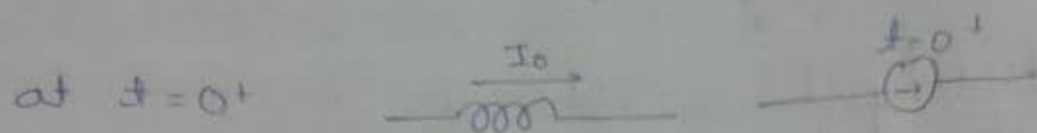at $t=0^-$ $\textcircled{B} \quad i_L(0^-) = \frac{3}{2} = 1.5 \text{ A}$




$$\frac{3 - V_L}{1} + \frac{3 - V_L}{2} = I_3 = 1.5$$

$$V_L = 2 = L \frac{di}{dt}$$

$\textcircled{D} \quad \frac{di}{dt} = \frac{2}{1} = 2 \text{ A/sec}$

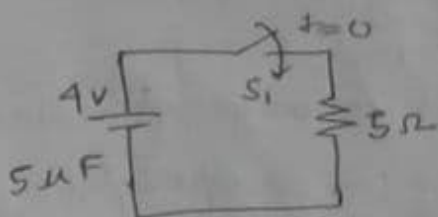Q.7 June-2016

In the ckt shown bellow, the initial capacitor voltage is 4V. Switch S_1 is closed at $t=0$. the charge in μC lost by the capacitor from $t=25 \mu\text{s}$ to $t=100 \mu\text{s}$ is _____ ?



$$V_c(0^-) = 4\text{V}$$

$$R i(t) + \frac{1}{C} \int_0^t i(t) dt + 4 = 0$$

$$\textcircled{A} \quad \frac{di(t)}{dt} + \frac{1}{C} i(t) = 0$$

$$\frac{di(t)}{dt} + \frac{1}{5 \times 5 \times 10^{-6}} i(t) = 0$$

$$i(t) = K e^{-40000t}$$

$$\text{at } t=0^+ \quad i(0^+) = -\frac{1}{5} = -0.2$$

$$K = -0.2$$

$$i(t) = -0.2 \cdot e^{-40000t}$$

$$V_R = R \cdot i(t) = -4 \cdot e^{-40000t}$$

$$V_C = 4 \cdot e^{-40000t}$$


$$\text{at } t = 25 \mu\text{s} \quad V_C = 1.47$$

$$t = 100 \mu\text{s} \quad V_C = 0.073$$

$$\Delta Q = C \cdot \Delta V = 5 \times 10^{-6} \times (1.47 - 0.073)$$

$$\Delta Q = 6.99 \mu\text{C}$$

(P.8) Example

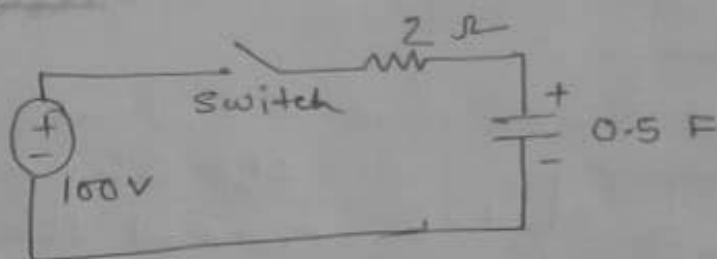

For fig the capacitor initially has a charge of 10 Coulomb. The current in the circuit 1 s after the switch S is closed will be _____ ?

$$Q = 10 \text{ C}$$

$$\text{initial voltage } V_0 = \frac{Q}{C} = \frac{10}{0.5} = 20 \text{ V}$$

$$\begin{aligned} \text{voltage across the capacitor} &= 100 + (20 - 100)e^{-t} \\ &= 100 - 80e^{-t} \end{aligned}$$

$$\tau = RC = 1$$


The current through the capacitor

$$\begin{aligned} I &= C \frac{dv(t)}{dt} = 0.5 \frac{d}{dt} (100 - 80e^{-t}) \\ &= 40 e^{-t} \end{aligned}$$

The current after one sec


$$i_c = 40.e^{-1} = 14.71 \text{ A}$$

(P.9)

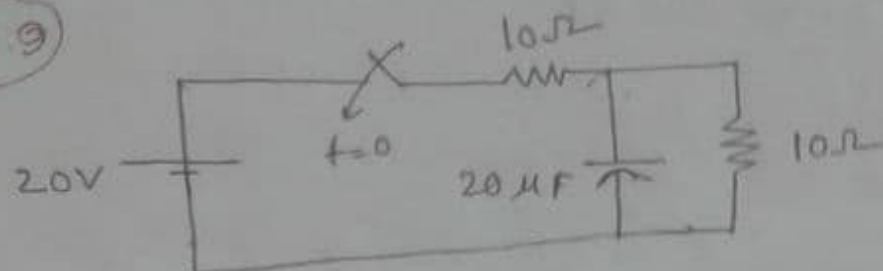


Initial capacitor voltage is zero.

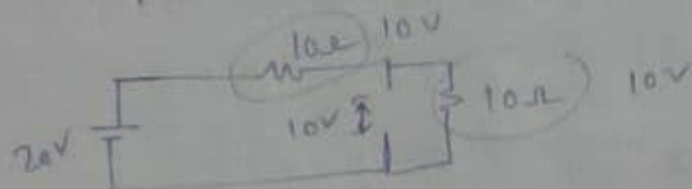Final steady state voltage across the capacitor is — ?



Ans - 10V


(P.10)

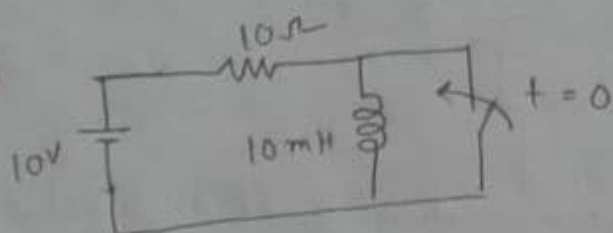

at $t = 0^+$
current through inductor — ?

for inductor, $i_L(0^-) = i_L(0^+)$
 $1 \text{ A} = 1 \text{ A}$

(P.11)

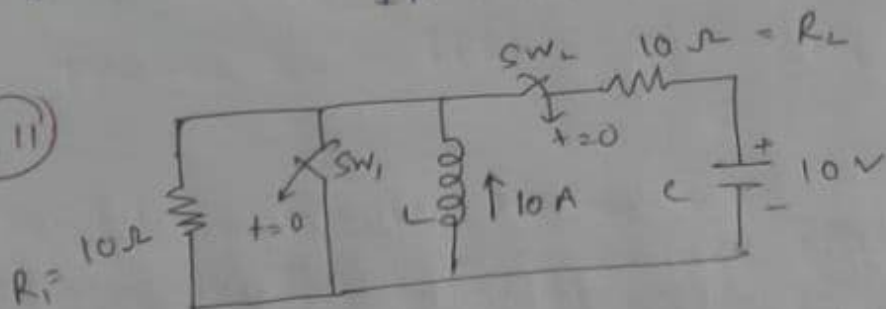


SW₁ is initially closed & SW₂ is open
 $I_{\text{inductor}} = 10 \text{ A}$

Capacitor is charged 10V with polarity

at $t = 0$ - SW₂ closed, SW₁ open.

find current through C and

Voltage across L at $t = 0^+$?

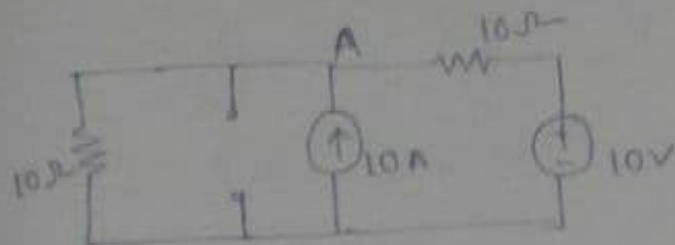

$$\frac{V_A}{10} + \frac{V_A - 10}{10} - 10 = 0$$

$$V_A = 55 \text{ V}$$

$$I_c = \frac{V_A - 10}{10} = 4.5 \text{ A}$$

$$4.5 \text{ A}, 55 \text{ V}$$

Ans.

16.09.2020

LAPLACE TRANSFORM

Laplace transform is an integral transform & transform having

$$g(\alpha) = \int_a^b f(t) \cdot k(\alpha, t) dt$$

is called integral transform.

$g(\alpha) \rightarrow$ is the function of α and it is o/p

$f(t) \rightarrow$ is the " of t " " i/p

$k(\alpha, t) \rightarrow$ " " " of both (α & t)

and it is known as integral kernel

$$\text{Let } f(t) \rightarrow \mathcal{L}\{f(t)\} = F(s) = \int_{-\infty}^{\infty} \underbrace{f(t)}_{\text{i/p}} \cdot \underbrace{e^{-st}}_{\text{integral kernel (I.K.)}} dt$$


s is a complex variable

$$s = \sigma + j\omega$$

σ is the damping factor

It tells about the stability

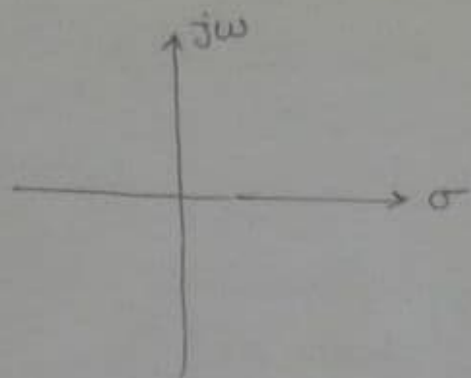$\omega \rightarrow$ is the angular frequency rad/sec



\mathcal{L} is a complex function

Bilateral \mathcal{L}

$$F(s) = \int_{-\infty}^{\infty} f(t) \cdot e^{-st} \cdot dt$$

If $f(t)$ such that $t \geq 0$

$$F(s) = \int_0^{\infty} f(t) \cdot e^{-st} \cdot dt$$

= unilateral \mathcal{L}

When deal with Bilateral \mathcal{L} it becomes important to maintain region of convergence (ROC) along with \mathcal{L}

ROC is the region of the s plane, where \mathcal{L} is finite in that region.

$$f(t) \rightarrow F(s)$$

$$\text{Inverse } \mathcal{L} = f(t) = \frac{1}{2\pi j} \int_{\sigma-j\omega}^{\sigma+j\omega} F(s) \cdot e^{st} \cdot ds$$

Condition for existence of \mathcal{L}

$$F(s) = \int_{-\infty}^{\infty} f(t) \cdot e^{-st} \cdot dt$$

$$= \int_{-\infty}^{\infty} f(t) \cdot e^{-(\sigma+j\omega)t} \cdot dt$$

$$= \int_{-\infty}^{\infty} \underbrace{f(t) \cdot e^{-\sigma t}}_{f_1(t)} \cdot e^{-j\omega t} \cdot dt$$

$$= \int_{-\infty}^{\infty} f_1(t) \cdot e^{-j\omega t} \cdot dt$$

where $f_1(t)$ is the absolutely integrable

signal.

Condition for signal to be absolutely integrable

$$\int_{-\infty}^{\infty} |f(t)| dt < \infty$$

$$\int_{-\infty}^{\infty} |f(t) \cdot e^{-\sigma t}| dt < \infty$$

This is the condition
for the existence
of X

↓
range of $\sigma \rightarrow$ ROC

ex-1 Find the ROC of signal, $f(t) = e^{2t} \cdot u(t)$


$$\begin{aligned} \int_{-\infty}^{\infty} |f(t) \cdot e^{-\sigma t}| dt &= \int_{-\infty}^{\infty} |e^{2t} u(t) \cdot e^{-\sigma t}| dt \\ &= \int_0^{\infty} |e^{(2-\sigma)t}| dt \end{aligned}$$

$$\begin{aligned} \int_{-\infty}^{\infty} |f(t) \cdot e^{-\sigma t}| dt &< \infty \\ &= \int_0^{\infty} |e^{(2-\sigma)t}| dt < \infty \end{aligned}$$

$$2 - \sigma < 0$$

$$-\sigma < -2$$
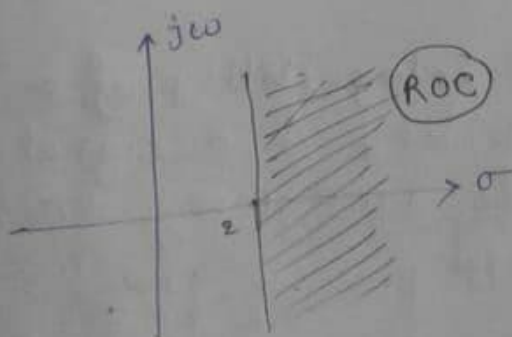
$$\textcircled{*} \sigma > 2 \rightarrow \text{range of } \sigma$$



$$f_1(t) \xrightarrow{\mathcal{L}} F_1(s)$$

$$f_2(t) \xrightarrow{\mathcal{L}} F_2(s)$$

$$F_1(s)$$


$$\downarrow$$

$$\sigma > 2$$

$$F_2(s)$$

$$\downarrow$$

$$\sigma < -1$$

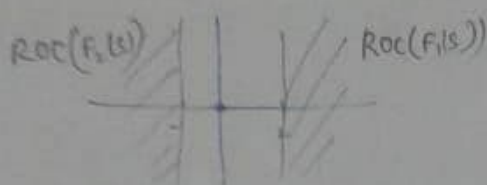

properties

① ROC doesnot include any poles


$$F(s) = \frac{1}{s+2}$$

$$s+2=0 \Rightarrow s=-2$$


$$F(-2) = \frac{1}{-2+2} = \frac{1}{0} = \infty$$

② For right sided signal, ROC is right side to the right most pole.

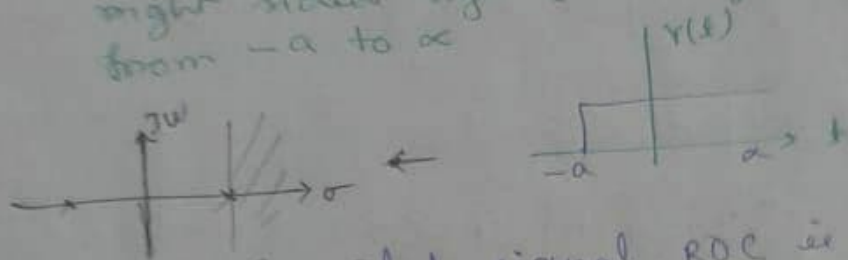
right sided signals having non-zero value from $-a$ to ∞



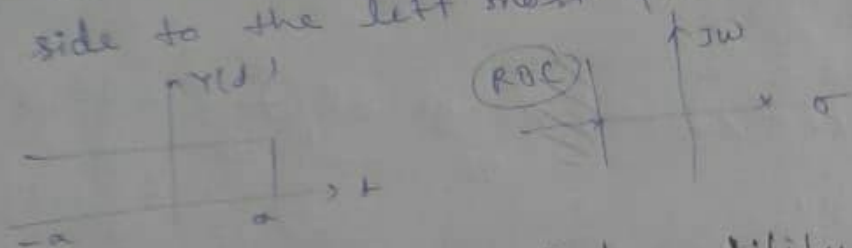
③ For left sided signal, ROC is left side to the left most pole



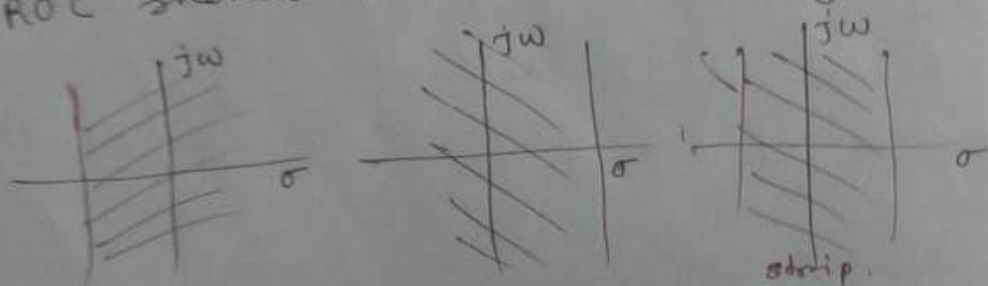④ For the absolute integrability of a signal or a stability of a signal, ROC should include imaginary axis.



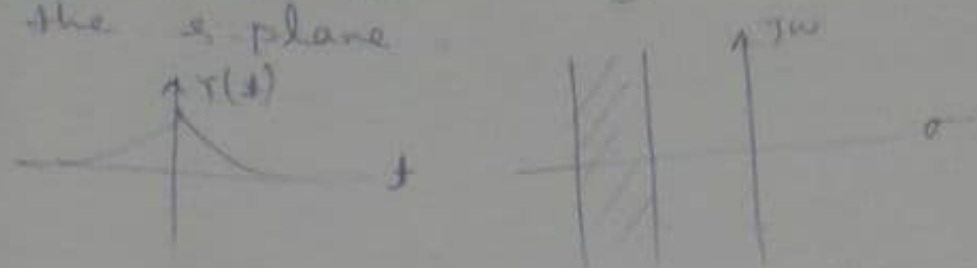- ⑤ For both sided signals ROC is a strip in the s -plane



- ⑥ For finite duration signal ROC is the entire s -plane excluding $s=0$ or $+\infty$ or $-\infty$



Step-1 - Compare σ with real part at the coefficient of t in power of e

Step-2 - check if the signal is left sided or right sided and decide $\langle \sigma \rangle$

ex-2

$$f(t) = e^{-at} u(-t)$$

σ = real part at s

Step-1 : coeff at $t = -a$
 $\sigma < -a$

ex-3 $f(t) = e^{(s+j3)t} u(-t-5)$ left sided

$$\sigma < 5$$

ex-4 $f(t) = e^{3t} u(t) + e^{-2t} u(-t)$

ROC 1

ROC 2

$u(-t)$
left sided

③

$$\sigma_2 < -2$$

ROC

$$\sigma_1 > 3$$

ROC 2

ROC 1



no common

ROC

↓

no

u(t) Right sided

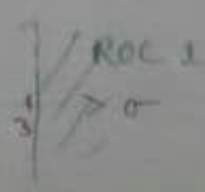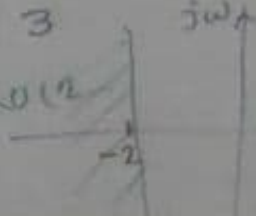

18092020

Properties of Laplace transform

$$\textcircled{1} \mathcal{L}[kf(t)] = kF(s)$$

$$\textcircled{2} \mathcal{L}[f_1(t) \pm f_2(t)] = F_1(s) \pm F_2(s)$$

$$\textcircled{3} \mathcal{L}\left[\frac{d}{dt}f(t)\right] = sF(s) - \lim_{t \rightarrow 0} f(t) \\ = sF(s) - f(0^+)$$

$$\mathcal{L}\left[\frac{d^2}{dt^2}f(t)\right] = s^2F(s) - sf(0^+) - f'(0^+) \\ = s^2F(s) - sf(0^+) - \frac{d}{dt}f(0^+)$$

$$\textcircled{4} \mathcal{L}\left[\int_0^t f(t) dt\right] = \frac{F(s)}{s}$$

$$\mathcal{L}\left[\int f(t) dt\right] = \mathcal{L}\left[\int_0^t f(t) dt + f^{-1}(0^+)\right] \\ = \frac{F(s)}{s} + \frac{f^{-1}(0^+)}{s}$$

where $f^{-1}(0^+)$ is the value of the integral $\int f(t) dt$ as t approaches zero.

$$\mathcal{L}\left[\int_0^{t_1} \int_0^{t_2} \int_0^{t_3} \dots \int_0^{t_n} f(t) dt_1 dt_2 \dots dt_n\right] = \frac{F(s)}{s^n}$$

$$\textcircled{5} \mathcal{L}[tf(t)] = -\frac{d}{ds}F(s)$$

$$\textcircled{6} \mathcal{L}\left[\frac{f(t)}{t}\right] = \int_s^\infty F(x) dx$$

$$\textcircled{7} \mathcal{L}[f(t-a)u(t-a)] = e^{-as}F(s)$$

$$(8) \mathcal{L}[e^{-at} f(t)] = F(s+a)$$

$$\mathcal{L}[e^{at} f(t)] = F(s-a)$$

(9) Initial value theorem

$$f(0+) = \lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} [s \cdot F(s)]$$

(10) Final value theorem

$$f(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [s \cdot F(s)]$$

(11) Convolution theorem

given two function $f_1(t)$ and $f_2(t)$ which are zero for $t < 0$

$$\text{if } \mathcal{L}[f_1(t)] = F_1(s)$$

$$\mathcal{L}[f_2(t)] = F_2(s)$$

$$\text{then } \mathcal{L}^{-1}[F_1(s) \cdot F_2(s)] = f_1(t) * f_2(t)$$

$$= \int_0^t f_1(t-\tau) \cdot f_2(\tau) d\tau$$

$$= \int_0^t f_1(\tau) \cdot f_2(t-\tau) d\tau$$

$$(12) \mathcal{L}[f(at)] = \frac{1}{|a|} F\left(\frac{s}{a}\right)$$

Laplace transform pairs

$f(t)$	$F(s)$
1 or $u(t)$	$1/s$
k	k/s
t	$1/s^2$
t^n	$\frac{n!}{s^{n+1}}$
$\delta(t)$	1
$e^{\pm at}$	$\frac{1}{s \mp a}$
$t e^{\pm at}$	$\frac{1}{(s \mp a)^2}$

$$\sin \omega t$$

$$\frac{\omega}{s^2 + \omega^2}$$

$$\cos \omega t$$

$$\frac{s}{s^2 + \omega^2}$$

$$e^{-at} \sin \omega t$$

$$\frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{+at} \sin \omega t$$

$$\frac{\omega}{(s-a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t$$

$$\frac{s+a}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cosh at$$

$$\frac{a}{s^2 - \omega^2}$$

$$\cosh at$$

$$\frac{s}{s^2 - \omega^2}$$

ex-1 $f(t) = u(t)$

$$F(s) = \int_{-\infty}^{\infty} f(t) \cdot e^{-st} dt$$

$$= \int_{-\infty}^{\infty} u(t) \cdot e^{-st} dt$$

$$= \int_0^{\infty} e^{-st} dt = \frac{e^{-st}}{-s} \Big|_0^{\infty} = \frac{1}{s}$$

ex-2 $f(t) = K + u(t)$

$$F(s) = \int_{-\infty}^{\infty} f(t) \cdot e^{-st} dt$$

$$= \int_{-\infty}^{\infty} K + u(t) \cdot e^{-st} dt$$

$$= K \cdot \int_0^{\infty} t \cdot e^{-st} dt$$

0

$$250 \times 12 + 12^2 \times 12500$$

$$250 \times 4 + 4^2 \times 0.5$$

$$9281664811 - PBC \text{ man}$$

$$\begin{aligned}
 &= k \left[t \frac{e^{-st}}{-s} \Big|_0^\infty \right] - k \int_0^\infty \frac{1 \cdot e^{-st}}{-s} dt \\
 &= 0 + \frac{k}{s} \int_0^\infty e^{-st} dt \\
 &= \frac{k}{s^2}
 \end{aligned}$$

$$a_0 \cdot \frac{d^n i}{dt^n} + a_1 \frac{d^{n-1} i}{dt^{n-1}} + \dots + a_{n-1} \frac{di}{dt} + a_n i = v(t)$$

$$\begin{aligned}
 I(s) &= \frac{\mathcal{L}\{v(t)\} + \text{Initial Condition}}{a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n} \\
 &= \frac{P(s)}{Q(s)}
 \end{aligned}$$

$$\begin{aligned}
 \text{Where } Q(s) &= a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n \\
 &= a_0 (s + s_1) \dots (s + s_n)
 \end{aligned}$$

① When all the roots of $Q(s)$ are simple

$Q(s) = 0$ then

$$I(s) = \frac{P(s)}{(s+s_1)(s+s_2)\dots(s+s_n)} = \frac{k_1}{s+s_1} + \frac{k_2}{s+s_2} + \dots + \frac{k_n}{s+s_n}$$

$$k_j = (s+s_j) \cdot I(s) \Big|_{s=-s_j}$$

ex-1 $F(s) = \frac{2}{(s-1)(s-2)}$

$$= \frac{C_1}{s-1} + \frac{C_2}{s-2}$$

$$\begin{aligned}
 C_1 &= (s-1) \cdot F(s) \Big|_{s=1} = (s-1) \frac{2}{(s-1)(s-2)} \Big|_{s=1} \\
 &= \frac{2}{1-2} = -2
 \end{aligned}$$

$$C_2 = (s-2) \cdot F(s) \Big|_{s=2} = \frac{2}{2-1} = 2$$

$$F(s) = \frac{-2}{s-1} + \frac{2}{s-2}$$

$$f(t) = -2e^{-t} + 2e^{+t} \quad [1 \text{ L T}]$$

② When some roots of $Q(s)$ are of multiple order.

if a root of $Q(s) = 0$, is of multiplicity r then

$$I(s) = \frac{P(s)}{(s+s_1)^r Q_1(s)} = \frac{K_{11}}{s+s_1} + \frac{K_{12}}{(s+s_1)^2} + \dots + \frac{K_{1r}}{(s+s_1)^r}$$

$$K_{1r} = (s+s_1)^r \cdot I(s) \Big|_{s=-s_1}$$

$$K_{1(r-1)} = \frac{d}{ds} [(s+s_1)^r \cdot I(s)] \Big|_{s=-s_1}$$

$$K_{1(r-2)} = \frac{1}{2!} \frac{d^2}{ds^2} [(s+s_1)^r \cdot I(s)] \Big|_{s=-s_1}$$

$$K_{11} = \frac{1}{(r-1)!} \frac{d^{r-1}}{ds^{r-1}} [(s+s_1)^r \cdot I(s)] \Big|_{s=-s_1}$$

example,

$$F(s) = \frac{2s+1}{(s+2)^3}$$

$$= \frac{C_{11}}{s+2} + \frac{C_{21}}{(s+2)^2} + \frac{C_{31}}{(s+2)^3}$$

$$C_{31} = (s+2)^3 \cdot F(s) \Big|_{s=-2}$$

$$= (s+2)^3 \cdot \frac{(2s+1)}{(s+2)^3} \Big|_{s=-2} = -2 \cdot 2 + 1 = -3$$

$$C_{21} = \frac{d}{ds} [(s+2)^3 \cdot F(s)] \Big|_{s=-2}$$

$$= \frac{d}{ds} \left[(s+2)^3 \cdot \frac{2s+1}{(s+2)^3} \right] \Big|_{s=-2}$$

$$= \frac{d}{ds} [2s+1] \Big|_{s=-2}$$

$$= 2$$

$$C_{11} = \frac{1}{(3-1)!} \frac{d^2}{ds^2} [(s+2)^3 F(s)] \Big|_{s=-2}$$

$$= \frac{1}{2!} \left[\frac{d^2}{ds^2} (2s+1) \right] \Big|_{s=-2} = 0$$

$$F(s) = \frac{2}{(s+2)^2} - \frac{3}{(s+2)^3}$$

③ Partial expansion when two roots of $Q(s)$ are of complex conjugate pair.

If two roots of $Q(s)=0$, which form a complex conjugate pair, then

$$I(s) = \frac{P(s)}{(s+\alpha+j\omega)(s+\alpha-j\omega)Q(s)} = \frac{K_1}{s+\alpha+j\omega} + \frac{K_1^*}{s+\alpha-j\omega} + \dots$$

$$K_1 = (s+\alpha+j\omega) I(s) \Big|_{s=-(\alpha+j\omega)}$$

K_1^* is a complex conjugate of K_1

example,

$$F(s) = \frac{s}{s^2+2s+2}$$

$$= \frac{C_1}{s+1+j1} + \frac{C_2}{s+1-j1}$$

$$s^2+2s+2=0$$

$$s = \frac{-2 \pm \sqrt{4-4}}{2}$$

$$= -1 \pm j1$$

$$C_1 = (s+1+j1) \cdot F(s) \Big|_{s=-1-j1}$$

$$= (s+1+j1) \cdot \frac{s}{(s+1+j1)(s+1-j1)} \Big|_{s=-1-j1}$$

$$= \frac{-1-j1}{-j2} = 0.5 - j0.5$$

$$C_2 = (s+1-j1) \cdot \frac{s}{(s+1+j1)(s+1-j1)} \Big|_{s=-1+j1}$$

$$= \frac{-1+j1}{j2} = 0.5 + j0.5$$

$$C_2 = C_1^*$$

example

$$F(s) = \frac{2s+3}{(s+2)(s^2+4s+8)}$$

roots of denominator
-2, -2 ± j2

$$F(s) = \frac{A}{s+2} + \frac{B}{s+2+j2} + \frac{B^*}{s+2-j2}$$

$$= \frac{A}{s+2} + \frac{BS+C}{s^2+4s+8} \quad (\text{alternative method})$$

$$= \frac{A(s^2+4s+8) + (s+2)(BS+C)}{(s+2)(s^2+4s+8)}$$

from which, $2s+3 = A(s^2+4s+8) + (s+2)(BS+C)$
 $= (A+B)s^2 + (4A+2B+C)s + (8A+2C)$

$$A+B=0, \quad 4A+2B+C=2, \quad 8A+2C=3$$

$$\therefore A = -\frac{1}{4}, \quad B = \frac{1}{4}, \quad C = \frac{5}{2}$$

$$F(s) = \frac{-1}{4(s+2)} + \frac{\frac{1}{4}s + \frac{5}{2}}{s^2+4s+8}$$

Q solve the differential equation.

$$x'' + 3x' + 2x = 0, \quad x(0^+) = 2, \quad x'(0^+) = -3$$

↓
taking Laplace transform

$$s^2 x(s) - s x(0^+) - x'(0^+) + 3s x(s) - 3x(0^+) + 2x(s) = 0$$

$$(s^2 + 3s + 2)x(s) = s x(0^+) + x'(0^+) + 3x(0^+)$$

$$(s^2 + 2s + 2)x(s) = 2s + 3$$

$$x(s) = \frac{2s+3}{s^2+2s+2} = \frac{2s+3}{(s+1)(s+2)} = \frac{k_1}{s+1} + \frac{k_2}{s+2}$$

$$k_1 = (s+1) \cdot x(s) \Big|_{s=-1} = \frac{(s+1)(2s+3)}{(s+1)(s+2)} \Big|_{s=-1} = \frac{-2+3}{-1+2} = 1$$



$$k_2 = (s+2) \cdot x(s) \Big|_{s=-2} = \frac{(s+2)(2s+3)}{(s+2)(s+1)} \Big|_{s=-2} = \frac{-4+3}{-2+1} = 1$$

$$x(s) = \frac{1}{s+1} + \frac{1}{s+2}$$

$$x(t) = \mathcal{L}^{-1}[x(s)] = \mathcal{L}^{-1}\left[\frac{1}{s+1} + \frac{1}{s+2}\right] = e^{-t} + e^{-2t}$$

Transformed circuit component Representations


① Independent sources:

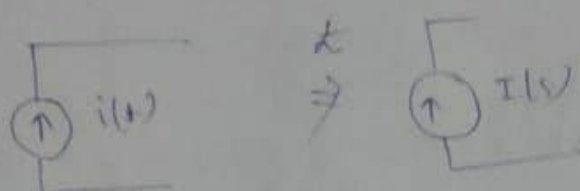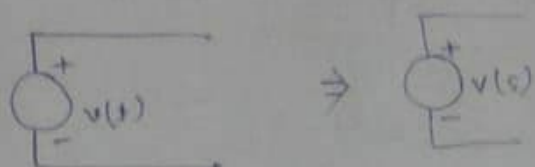

② Resistance

$$V_R(t) = R \cdot i_R(t)$$

$$V_R(s) = R I_R(s)$$


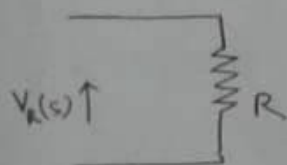


③ Inductance

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$V_L(s) = L [s I_L(s) - i_L(0^+)]$$

$$= L s I_L(s) - L i_L(0^+)$$

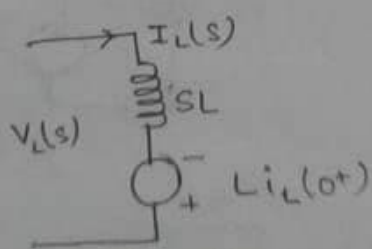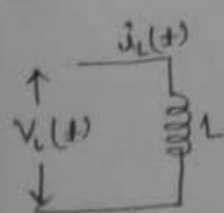


time domain

s-domain


$$i_L(t) = \frac{1}{L} \int_0^t V_L(t) dt + i_L(0^+)$$
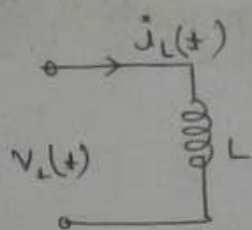
$$I_L(s) = \frac{V_L(s)}{sL} + \frac{i_L(0^+)}{s}$$



time domain

\Rightarrow

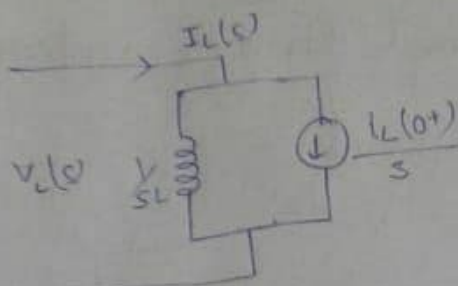


s-domain


④ Capacitor

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$I_c(s) = sC v_c(s) - C v_c(0^+)$$

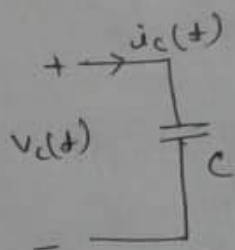


\Rightarrow

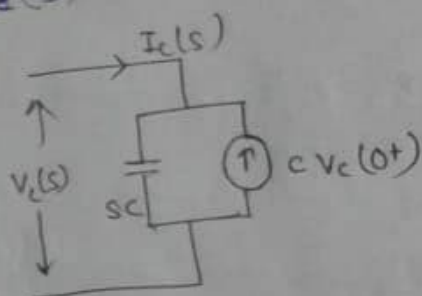


$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + v_c(0^+)$$

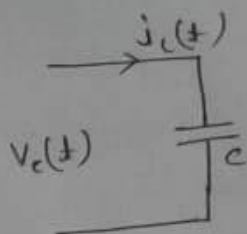
$$v_c(s) = \frac{I_c(s)}{Cs} + \frac{v_c(0^+)}{s}$$



\Rightarrow

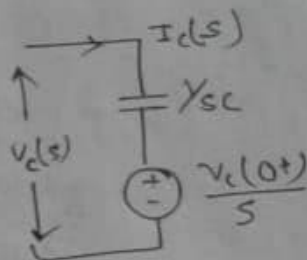

ex-1:

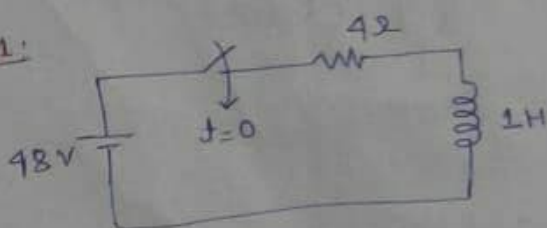

Assume the initial current through the inductor is 3A. $i(t)$ $t \geq 0$

Also draw the s-domain representation of the circuit

Apply KVL

$$R i(t) + L \frac{di(t)}{dt} = 48$$

$$R I(s) + L [s I(s) - i_L(0^+)] = \frac{48}{s}$$

$$4 I(s) + 1 [s I(s) - 3] = \frac{48}{s}$$

$$I(s) = \frac{3s + 48}{s(s+4)}$$

$$= \frac{K_1}{s} + \frac{K_2}{s+4}$$

$$K_1 = s \cdot I(s) \Big|_{s=0} = 12$$

$$K_2 = (s+4) I(s) \Big|_{s=-4} = -9$$

$$I(s) = \frac{12}{s} - \frac{9}{s+4}$$

$$i(t) = (12 - 9 \cdot e^{-4t}) \text{ A}$$

or.

$$4 i(t) + 1 \frac{di(t)}{dt} = 48$$

$$\frac{di(t)}{dt} + 4 i(t) = 48$$


$$i(t) = \frac{48}{4} + K \cdot e^{-4t}$$

$$i_L(0^-) = 3 \text{ A}$$

$$3 = 12 + K$$

$$K = -9$$

$$i(t) = 12 - 9 \cdot e^{-4t}$$

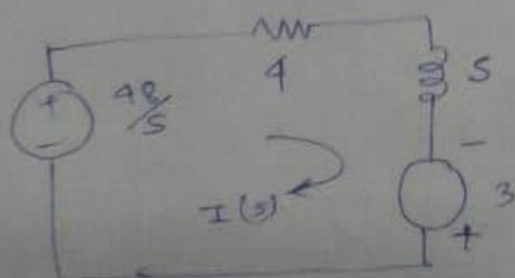


$$V = \frac{48}{s} + 3$$

$$Z = 4 + s$$

$$I = (\frac{48}{s} + 3) / (s+4)$$

s-domain

ex-2

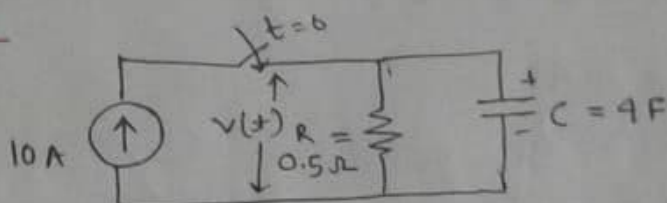

assume initial voltage across the capacitor is 2V

draw the s-domain capacitor.

apply KCL

$$\frac{v(t)}{R} + C \frac{dv(t)}{dt} = 0$$

$$\frac{V(s)}{R} + C [sV(s) - v(0^+)] = 10/s$$

$$2V(s) + 4 [sV(s) - 2] = 10/s$$

$$V(s) = \frac{8s + 10}{s(4s + 2)}$$

$$= \frac{2s + 2.5}{s(s + 0.5)}$$


$$= \frac{K_1}{s} + \frac{K_2}{s + 0.5}$$

$$K_1 = s \cdot V(s) \Big|_{s=0} = 5$$


$$K_2 = (s + 0.5) V(s) \Big|_{s=-0.5} = -3$$

$$V(s) = \frac{5}{s} - \frac{3}{s + 0.5}$$

$$v(t) = (5 - 3e^{-0.5t})V$$

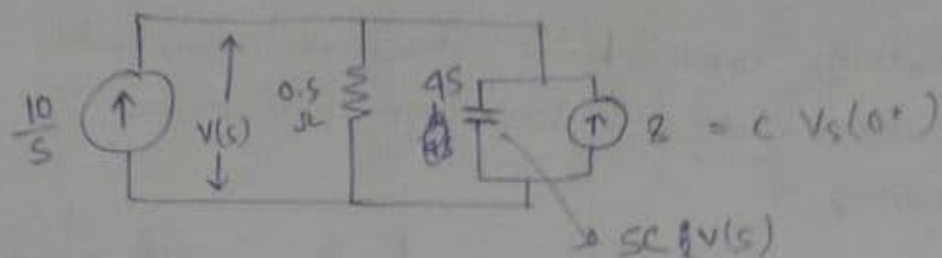

ex-3

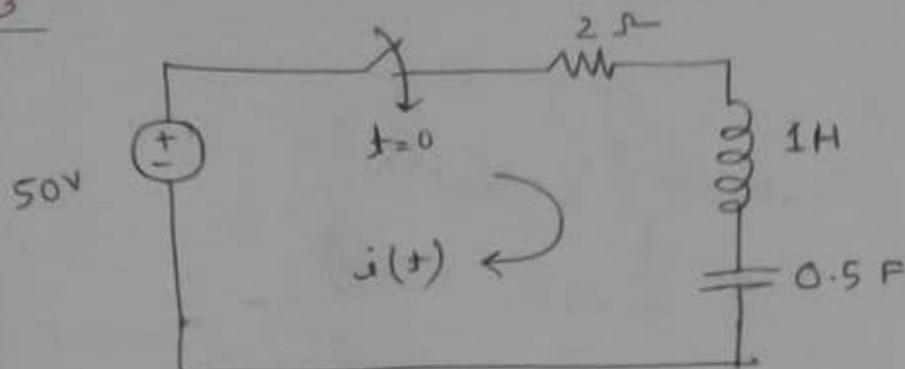

no initial charge in capacitor.

Find $i(t)$, $t \geq 0$, all initial conditions are zero.

KVL, $2 i(t) + 1 \frac{di(t)}{dt} + \frac{1}{0.5} \int i(t) dt = 50$

$$2 i(t) + \frac{di(t)}{dt} + 2 \int i(t) dt = 50$$

$$2 I(s) + s I(s) - i(0^+) + 2 \frac{I(s)}{s} = 50/s$$

$$I(s) = \frac{50}{s^2 + 2s + 2} = \frac{50}{(s+1)^2 + 1}$$

$$i(t) = 50 e^{-t} \sin t \quad A$$

Ex - using convolution theorem evaluate the inverse Laplace transform for the following

(i) $\frac{1}{(s+a)^2}$ (ii) $\frac{1}{s(s+a)}$ (iii) $\frac{1}{(s+a)(s+b)}$ (iv) $\frac{1}{(s^2+1)^2}$

$$\textcircled{i} \quad F(s) = \frac{1}{(s+a)^2} = \frac{1}{(s+a)(s+a)}$$

$$= F_1(s) \cdot F_2(s)$$

Where $F_1(s) = \frac{1}{s+a}$ $F_2(s) = \frac{1}{s+a}$

$f_1(t) = e^{-at}$ $f_2(t) = e^{-at}$

$$\mathcal{L}^{-1}[F_1(s) \cdot F_2(s)] = f_1(t) * f_2(t)$$

$$= \int_0^t f_1(\tau) \cdot f_2(t-\tau) \cdot d\tau$$

$$= \int_0^t e^{-a\tau} \cdot e^{-a(t-\tau)} d\tau$$

$$= e^{-at} \int_0^t e^{-a\tau} e^{a\tau} d\tau$$

$$= e^{-at} \int_0^t d\tau = t e^{-at}$$

$$f(t) = e^{-at} \int_0^t d\tau = t e^{-at}$$

$$f(t) \rightarrow t e^{-at}$$

(11)

$$F(s) = \frac{1}{s(s+a)}$$

$$f(t)$$

$$F_1(s) = \frac{1}{s}$$

$$F_2(s) = \frac{1}{s+a}$$

$$f_1(t) = u(t)$$

$$f_2(t) = e^{-at}$$


$$\begin{aligned} f(t) &= \int_0^t f_1(\tau) f_2(t-\tau) d\tau \\ &= \int_0^t e^{-a(t-\tau)} d\tau \\ &= e^{-at} \int_0^t e^{a\tau} d\tau \\ &= \frac{1 - e^{-at}}{a} \end{aligned}$$

P. ① The output response of a system is denoted by $y(t)$, as its Laplace transform is given by $Y(s) = \frac{10}{s(s^2 + s + 100\sqrt{2})}$

The steady state value of $y(t)$ is —?





$$Y(s) = \frac{10}{s(s^2 + s + 100\sqrt{2})}$$


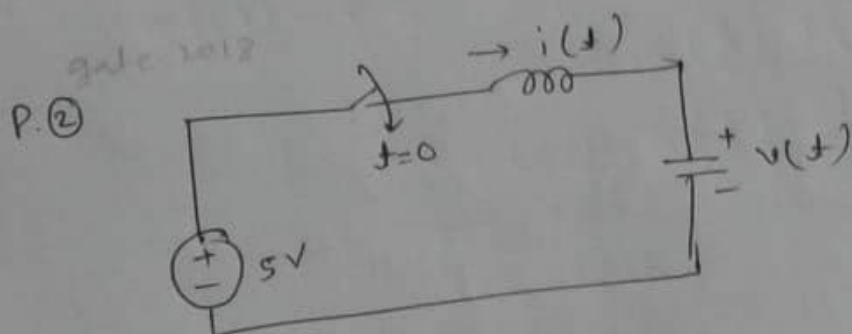
$$\begin{aligned} y(t) &= \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} Y(s) \\ &= \lim_{s \rightarrow 0} s \frac{10}{s(s^2 + s + 100\sqrt{2})} \\ &= \frac{1}{10\sqrt{2}} \end{aligned}$$



$$i_L(0) = 0, \quad v_L(0) = 0$$

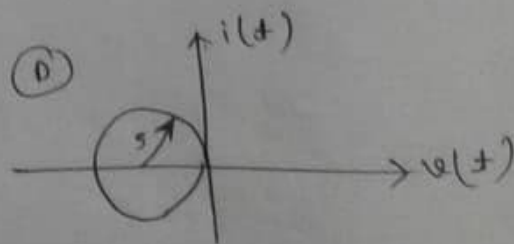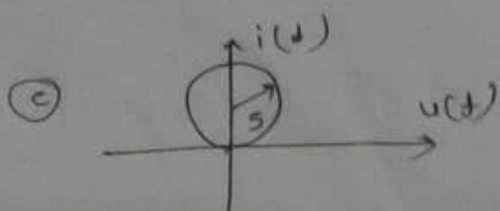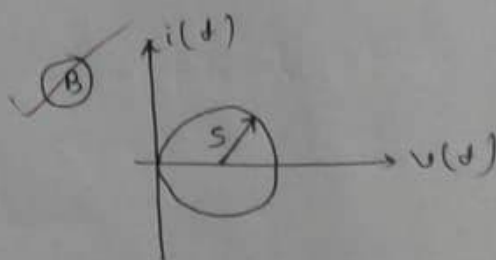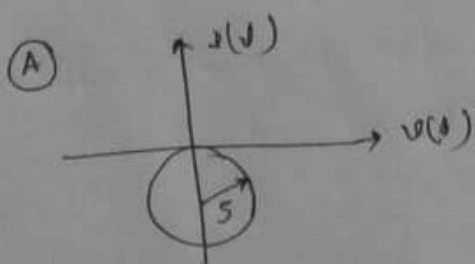which one of the following loci presents the plot of $i(t)$ vs $v(t)$



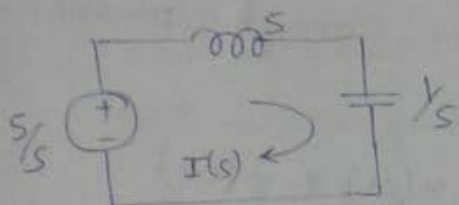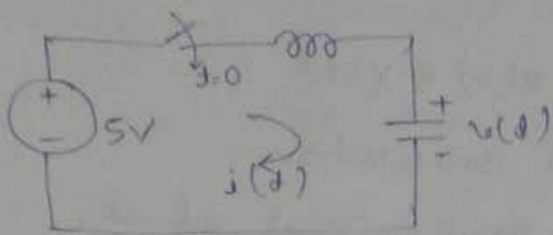





$$I(s) = \frac{5/s}{s + 1/s} = \frac{5}{s^2 + 1}$$

$$i(t) = 5 \sin t$$

$$v(t) = \frac{1}{C} \int_0^t i(t) dt$$

$$= 1 \cdot \int_0^t 5 \sin t dt$$

$$= 5(1 - \cos t)$$

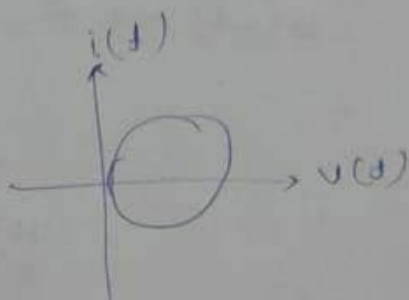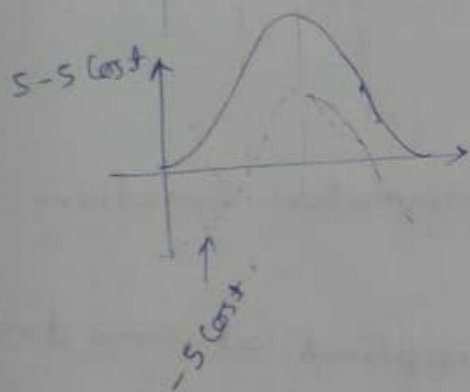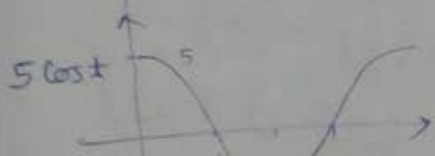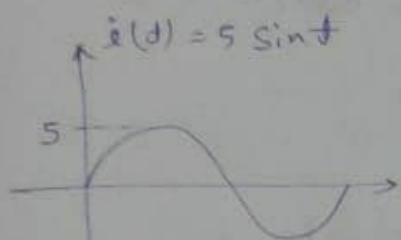

$$v(t) = 5(1 - \cos t)$$

$$= 5 - 5 \cos t$$

$$= 5 - 5 \left(\cos^2 t - \sin^2 t \right)$$

$$= 5 - 5 \cos^2 t + 5 \sin^2 t$$

$$= 5 - 5 \cos^2 t + 5(1 - \cos^2 t)$$

$$= 5 - 5 \cos^2 t + 5 - 5 \cos^2 t$$

$$= 10 - 10 \cos^2 t$$

$$= 10(1 - \cos^2 t)$$

$$= 10 \sin^2 t$$

$$a + b = 10$$

$$v(t) = 10 \sin^2 t$$

$$= 10$$

$$\gamma(t) = u(t) - 2e^{-t}u(t)$$

$$t = 1.5 \text{ sec. } \gamma(1.5) = 1 - 2e^{-1.5} \\ = 1 - 0.446 = \underline{\underline{0.554}}$$

P(5) The Laplace transform of $f(t) = e^{2t} \sin t \cdot u(t)$ is

$$F(s) = \frac{5}{(s-2)^2 + 25} = \frac{5}{s^2 - 4s + 29}$$

P. ③. Let $z(t) = x(t) * y(t)$

* denotes convolution

Let c be a positive real-valued constant choose the correct expression for $z(ct)$

- ☒ (A) $c \cdot x(ct) * y(ct)$ (B) $x(ct) * y(ct)$
☐ (C) $c \cdot x(t) * y(t)$ (D) $c \cdot x(ct) * y(t)$

Ans. $z(t) = x(t) * y(t)$
 $z(s) = X(s) \cdot Y(s)$

$$\begin{aligned}
 z(ct) &\rightarrow Z \rightarrow \frac{1}{c} \cdot z\left(\frac{s}{c}\right) \\
 &= \frac{1}{c} \cdot X\left(\frac{s}{c}\right) \cdot Y\left(\frac{s}{c}\right) \\
 &= c \cdot \frac{1}{c} \cdot X\left(\frac{s}{c}\right) \cdot \frac{1}{c} \cdot Y\left(\frac{s}{c}\right)
 \end{aligned}$$

ILT ↙

$$c \cdot x(ct) * y(ct)$$

P. ④ For a system having transfer function

$$G(s) = \frac{-s+1}{s+1}$$

A unit step input is applied at time $t=0$
 The value of the response of the system at $t=1.5s$ _____ ?

$$G(s) = \frac{-s+1}{s+1}$$

System output $Y(s) = G(s) \cdot \frac{1}{s}$

$$= \frac{-s+1}{s+1} \cdot \frac{1}{s}$$

$$Y(s) = \frac{1}{s} - \frac{2}{s+1}$$