

# Design of Counters

October 28, 2020

# Design of Binary Counter of any Arbitrary Modulus

- ▶ Suppose we want to design a modulo  $M$ -counter for any arbitrary value of  $M$ .
- ▶ Counter will count from 0 to  $M-1$ , and back to 0.
- ▶ Assume that flip-flops have clear (CLR) inputs.

# Basic Idea

- ▶ We first design a ripple counter with  $\lceil \log_2 M \rceil$  stages.
- ▶ Then, we will design a gating circuit which takes input from the outputs of the counter and generates a signal whenever the value reaches  $M$ .
- ▶ Connect the output of the gating circuit to CLR inputs of the flip-flops.

# Modulo - 6 Ripple Counter

- ▶ The number of stages =  $\lceil \log_2 M \rceil = 3$
- ▶ The desired count sequences are as follows:  
000 001, 010, 011, 100, 101, 000,.....
- ▶ From the state 101, instead of going to the state 110, we have to bring back to 000.


 


Figure: Circuit diagram of a Mod-6 Ripple Counter.
 
# Cascading of Ripple counters

- If a mod-M counter and a mod-N counter are connected in cascade, the combination will count modulo-MN.



# Lockout

- ▶ For a Mod-5 counter, logic states  $Q_2Q_1Q_0 = 101, 110,$  and  $111$  are not used. Suppose that, by chance, the counter happened at some point to find itself in any one of these unused states.
- ▶ Such a situation might develop as a result of external noise affecting the state of a flip-flop.
- ▶ we do not know the next state for a unused state. Hence, there is the further possibility that when a flip-flop is thrown into an unused state, the counter might cycle from unused state to unused state, never arriving at a used state.
- ▶ A counter whose unused states have this feature is said to suffer from *lockout*.

## Example of synchronous Counter

- Design a Mod-5 synchronous counter such that if the unused states  $Q_2Q_1Q_0 = 101, 110,$  or  $111$  occur, the next clock pulse will reset the counter  $Q_2Q_1Q_0 = 000$ .

The excitation table of the circuit for the aforesaid problem is given below:

| Counter state S | $Q_2$ | $Q_1$ | $Q_0$ | $J_2$ | $K_2$ | $J_1$ | $K_1$ | $J_0$ | $K_0$ |
|-----------------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0               | 0     | 0     | 0     | 0     | X     | 0     | X     | 1     | X     |
| 1               | 0     | 0     | 1     | 0     | X     | 1     | X     | X     | 1     |
| 2               | 0     | 1     | 0     | 0     | X     | X     | 0     | 1     | X     |
| 3               | 0     | 1     | 1     | 1     | X     | X     | 1     | X     | 1     |
| 4               | 1     | 0     | 0     | X     | 1     | 0     | X     | 0     | X     |
| US              | 1     | 0     | 1     | X     | 1     | 0     | X     | X     | 1     |
| US              | 1     | 1     | 0     | X     | 1     | X     | 1     | X     | 1     |
| US              | 1     | 1     | 1     | X     | 1     | X     | 1     | X     | 1     |

The Boolean functions for the flip-flop inputs are as follows:

$$J_2 = Q_1Q_0, K_2 = 1, J_1 = \overline{Q_1}Q_0, K_1 = Q_2 + Q_0 = \overline{\overline{Q_2}}\overline{\overline{Q_0}}$$

$$J_0 = \overline{Q_2}, K_0 = 1$$

## AND COUNTERS 341

FIGURE 10.11.2

Figure: Timing Diagram