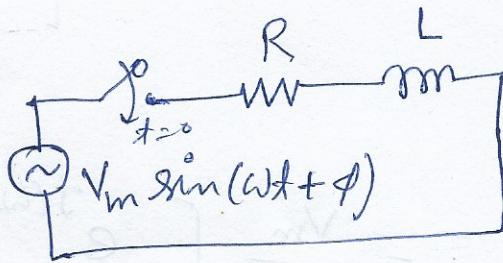


Transient Response of series R-L circuit having
Sinusoidal Excitation.

Applying KVL

$$L \frac{di(t)}{dt} + R i(t) = V_m \sin(\omega t + \phi)$$



$$\Rightarrow \frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_m}{L} \sin(\omega t + \phi)$$

This is a non-homogeneous equation, the current $i(t)$ consists of the sum of complementary function $i_c(t)$ and particular integral $i_p(t)$

$$i_t = i_c + i_p$$

The complementary function of equation is

$$i_c = K e^{-R_L t}$$

and the integral particular integral of equation

$$\left[\frac{dy(t)}{dt} + py(t) = Q \Rightarrow y(t) = e^{-pt} \int Q e^{pt} dt + K e^{-pt} \right]$$

$$i_p(t) = e^{-R_L t} \int \frac{V_m}{L} \sin(\omega t + \phi) e^{+R_L t} dt$$

$$= e^{-R_L t} \int \frac{V_m}{L} \left[\frac{e^{j(\omega t + \phi)}}{2j} - \frac{e^{-j(\omega t + \phi)}}{2j} \right] e^{+R_L t} dt$$

$$\sin \theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}$$


$$= \frac{e^{-R_L t} \cdot V_m}{2jL} \int \left(e^{j(\omega t + \phi) + R_L t} - e^{-j(\omega t + \phi) + R_L t} \right) dt$$

$$= \frac{e^{-\frac{R}{L}t} \cdot V_m}{2jL} \left[\frac{e^{j(\omega t + \phi) + \frac{R}{L}t}}{j\omega + \frac{R}{L}} - \frac{e^{-j(\omega t + \phi) + \frac{R}{L}t}}{-j\omega + \frac{R}{L}} \right]$$

$$= \frac{V_m}{2jL} \left[\frac{e^{j(\omega t + \phi)}}{\frac{R}{L} + j\omega} - \frac{e^{-j(\omega t + \phi)}}{\frac{R}{L} - j\omega} \right]$$

$$= \frac{V_m}{2jL} \left[\frac{e^{j(\omega t + \phi)} (\frac{R}{L} - j\omega) - e^{-j(\omega t + \phi)} (\frac{R}{L} + j\omega)}{(\frac{R}{L} + j\omega)(\frac{R}{L} - j\omega)} \right]$$
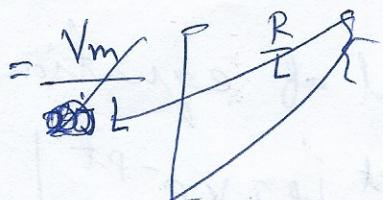
$$= \frac{V_m}{2jL} \left[\frac{\frac{R}{L} \{ e^{+j(\omega t + \phi)} - e^{-j(\omega t + \phi)} \} - j\omega \{ e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)} \}}{(\frac{R}{L})^2 + (\omega)^2} \right]$$



$$= \frac{V_m}{L \left\{ \frac{R^2}{L^2} + \omega^2 \right\}} \left[\frac{\frac{R}{L} \{ e^{j(\omega t + \phi)} - e^{-j(\omega t + \phi)} \}}{2j} - j\omega \left\{ \frac{e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)}}{2j} \right\} \right]$$

$$= \frac{V_m}{R^2 + \omega^2 L^2} \left[R \sin(\omega t + \phi) - \omega L \cos(\omega t + \phi) \right]$$

Let $R = C \cos \theta$, $-\omega L = C \sin \theta$.

$$C = \sqrt{R^2 + (\omega L)^2}$$

$$\theta = -\tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$i_p(t) = \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$= \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot [C \sin(\omega t + \phi + \theta)]$$

$$= \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot \sqrt{R^2 + \omega_L^2} \cdot \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$= \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$\therefore i(t) = K e^{-R_L t} + \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$


$i(0^+) = 0$, (inductor behaves as an open circuit at switching)

$$0 = \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot \sin(\phi - \tan^{-1} \frac{\omega L}{R}) + K$$

$$\therefore K = - \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot \sin(\phi - \tan^{-1} \frac{\omega L}{R})$$

$$\therefore i(t) = \frac{V_m}{\sqrt{R^2 + \omega_L^2}} \cdot [\sin(\omega t + \phi + \theta) - \sin(\phi + \theta) \cdot e^{-R_L t}]$$

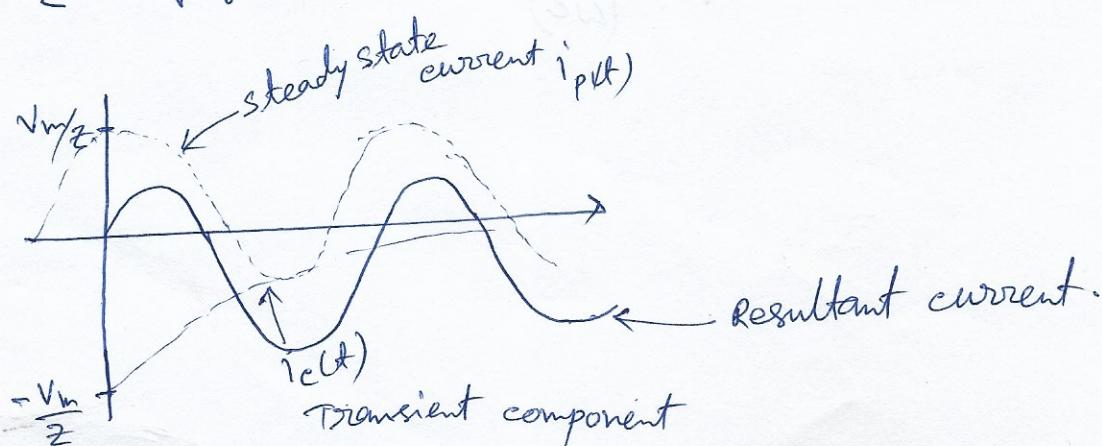
$$Z = \sqrt{R^2 + \omega_L^2}, \quad \theta = -\tan^{-1} \frac{\omega L}{R}$$



Transient Response of series R-C circuit Having Sinusoidal excitation.

Applying KVL
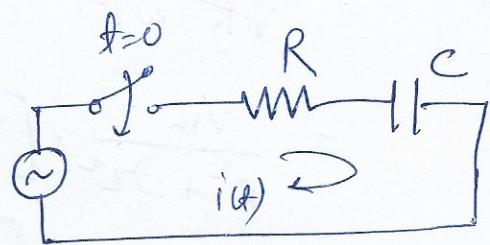
$$R i(t) + \frac{1}{C} \int_0^t i(t) dt + V_c(0^+) = V_m \sin(\omega t + \phi)$$



$$V = V_m \sin(\omega t + \phi)$$

on differentiating, we get

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = \frac{V_m \omega}{R} \cos(\omega t + \phi)$$

General solution of this differential equation is

$$i(t) = i_c(t) + i_p(t)$$

$$= K e^{-\frac{t}{RC}} + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

Since capacitor behaves as a short circuit at switching

$$i(0^+) = \frac{V_m \sin \phi}{R}$$

$$\text{or, } \frac{V_m \sin \phi}{R} = K + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

$$\text{or, } K = \frac{V_m \sin \phi}{R} - \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

$$\therefore i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin \left(\phi + \tan^{-1} \frac{1}{\omega CR} \right) \right] e^{-t/RC} + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin \left(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR} \right)$$

$$\text{or. } i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m \sin(\phi + \theta)}{Z} \right] e^{-t/RC} + \frac{V_m}{Z} \sin(\omega t + \phi + \theta)$$

$$\theta = \tan^{-1} \left(\frac{1}{\omega CR} \right), Z = \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

Example 1:- A 50Hz 300V (peak value) sinusoidal voltage is applied at $t=0$ to a series R-L circuit having resistance 2.5Ω and inductance 0.1H. Find an expression of current at any instant t . Also, calculate the value of the transient current, steady state current and resultant current 0.01 sec. after switching on.

Solution:- Impedance of R-L circuit.

$$Z = \sqrt{(2.5)^2 + (2\pi \times 50 \times 0.1)^2} = 31.5 \Omega$$

$$\text{Transient current } i_{ct}(t) = K e^{-R_L t} = K e^{-25t}$$

$$\text{Steady state current } i_{ps}(t) = \frac{V_m}{Z} \sin \left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} \right)$$

$$= \frac{300}{31.5} \sin(314t - 85.45^\circ)$$

Since voltage is applied at $t=0$, i.e. $\phi=0$ and $\tan^{-1} \left(\frac{314 \times 0.1}{2.5} \right) = 85.45^\circ$

$$= 9.52 \sin(314t - 1.49) \quad [\text{since } 85.45^\circ = 1.49 \text{ rad}]$$

$$\therefore i(t) = i_c(t) + i_{p(t)}$$

$$= Ke^{-25t} + 9.52 \sin(314t - 1.49)$$

Since $i(0^+) = 0$

$$0 = K + 9.52 \sin(-1.49)$$

$$\text{or, } K = 9.49$$

$$\therefore i(t) = 9.49 e^{-25t} + 9.52 \sin(314t - 1.49)$$

$$\text{at } t=0.01 \text{ sec } i(t) = 9.49 e^{-25 \times 0.01} = 7.39 \text{ A}$$

$$i_p(t) = 9.52 \sin(314 \times 0.01 - 1.49) = 9.49 \text{ A}$$

$$i(t) = i_c(t) + i_p(t) = 16.88 \text{ A}$$

Problem 2 A voltage $v = 300 \sin 314t$ is applied at $t = 2.14 \text{ msec}$ to a series R-C circuit having resistance 10Ω and capacitance $200 \mu\text{F}$. Find an expression for current. Also, find the value of current 1 msec after switching on.

Solu: It may be noted that the voltage is not applied at $t=0$, but at ϕ where $\phi = 2.14 \text{ msec}$

$$= 2.14 \times 10^{-3} \times 314 = 0.672 \text{ rad.}$$

\therefore

Impedance of R-C circuit

$$Z = \sqrt{(10)^2 + \left(\frac{1}{314 \times 200 \times 10^{-6}}\right)^2} = 18.8 \Omega$$

Transient current

$$i_c(t) = K e^{-t/RC} = K e^{-\frac{t}{10 \times 200 \times 10^6}} = K e^{-500t}$$

Steady state current

$$i_p(t) = \frac{V_m}{Z} \sin(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR})$$

$$= \frac{300}{18.8} \sin \left[314t + 0.672 + \tan^{-1} \left(\frac{1}{314 \times 200 \times 10^6 \times 10} \right) \right]$$

$$= 15.96 \sin(314t + 0.672 + 1.59)$$

Therefore $i(t) = i_c(t) + i_p(t)$

$$= K e^{-500t} + 15.96 \sin(314t + 0.672 + 1.59)$$

since capacitor behaves as a short-circuit at switching

$$\therefore i(2.14 \text{ msec}) = \frac{300 \times \sin(314 \times 2.14 \times 10^{-3})}{10} = 18.67 \text{ A}$$

Hence we get

$$18.67 = K(1) + 15.96 \sin(0.672 + 1.59)$$

$$\text{or, } K = 18.67 - \frac{15.86}{12.29} = 6.38 \cancel{2.808} 2.81$$

Therefore, the required expression of current is given by

$$i(t) = 6.38 e^{-500t} + 15.96 \sin(314t + 2.262)$$

after 1 msec. the current becomes.


$$i = 6.38 e^{-500 \times 10^{-3}} + 15.96 \sin(314 \times 10^{-3} + 2.262)$$

$$= \frac{1.70}{3.87} + \frac{14.53}{8.55} = \cancel{12.42} 1.682$$

$$= 16.23 \text{ A}$$

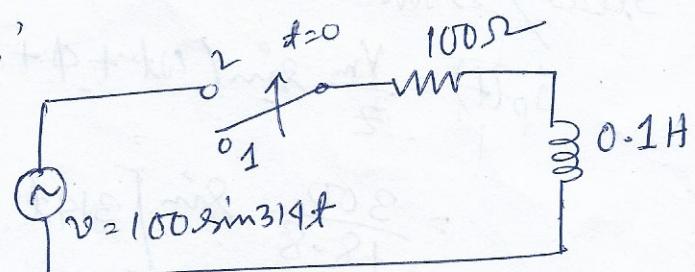Problem 3 :- obtain the current at $t=0$ if a.c. voltage v is applied when the switch S is moved to 2 from 1 at $t=0$. Assume a steady state current of 1A in the LR circuit when the switch was at position 1.

Ans) At position 1 of the switch 's' the steady state current in the circuit is 1A, $i(0^-) = 1A = i(0^+)$



$$Z = R + jX_L = 100 + j2\pi \times 50 \times 0.1 \\ = 104.8 \angle 17.47^\circ$$

Applying KVL in the RL circuit

$$R.i + L \frac{di}{dt} = v$$

$$\Rightarrow 100i + 0.1 \frac{di}{dt} = 100 \sin 314t$$

$$\Rightarrow \frac{di}{dt} + 10^3 i = 10^3 \sin 314t$$

$$\Rightarrow i_c = C e^{-\frac{R}{L}t} = C e^{-\frac{100}{0.1}t} = C e^{-1000t}$$

$$i_p = \frac{V_m}{Z} \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R})$$

$$= \frac{100}{104.8} \sin(314t - 17.47^\circ) \quad [\phi = 0]$$

$$= 0.954 \sin(314t - 0.304)$$

$$\therefore i = i_c + i_p = C e^{-1000t} + 0.954 \sin(314t - 0.304)$$

$$C = 1.28$$

problem 4 :- In a series R-L-C circuit, $R=5\Omega$, $L=1H$ and $C=1F$. A d.c. voltage of 20V is applied at $t=0$, obtain $i(t)$.

Solution:- Applying at KVL yields, in the series RLC circuits.

$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V \quad \text{--- (1)}$$

$$\Rightarrow L \cdot \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$$

$$\Rightarrow LP^2 + RP + \frac{1}{C} = 0 \Rightarrow P^2 + 5P + 1 = 0$$

$$P_1, P_2 = \frac{-5 \pm \sqrt{25-4}}{2} = \frac{-5 \pm 4.58}{2} = -0.21, -4.79$$

$$P_1, P_2 = \frac{-5 \pm \sqrt{25-4}}{2} = \frac{-5 \pm 4.58}{2} = -0.21, -4.79$$

$$P_1, P_2 = \frac{-5 \pm \sqrt{25-4}}{2} = \frac{-5 \pm 4.58}{2} = -0.21, -4.79$$

The solution becomes, $i(t) = K_1 e^{-0.21t} + K_2 e^{-4.79t}$

As current in inductance cannot change instantaneously and also the voltage across the capacitor does not change instantaneously. $i(0^+) = 0$ and $\frac{1}{C} \int i dt = 0$

Thus from (1) $L \frac{di}{dt} = V$ (at $t=0^+$)

$$\frac{di}{dt}(0^+) = \frac{V}{L} = \frac{20}{1} = 20 \text{ A/sec.}$$

Again substituting $i=0$ at $t=0^+$ in (2)

$$0 = K_1 e^{-0.21 \times 0} + K_2 e^{-4.79 \times 0}$$

$$0 = K_1 + K_2$$

Again differentiating equation 2

$$\frac{di}{dt} = -0.21 K_1 e^{-0.21t} - 4.79 K_2 e^{-4.79t}$$

$$\text{at } t=0^+, 20 = -0.21 K_1 e^{-0.21t} - 4.79 K_2 e^{-4.79t}$$

$$20 = -0.21 K_1 - 4.79 K_2$$


$$20 = -4.58 K_2$$

$$[K_2 = -K_1]$$

$$K_2 = -4.37 \text{ Hence } K_1 = 4.37$$

$$i(t) = (4.37 e^{-0.4t} - 4.37 e^{-4.37t}) A$$

problem 5

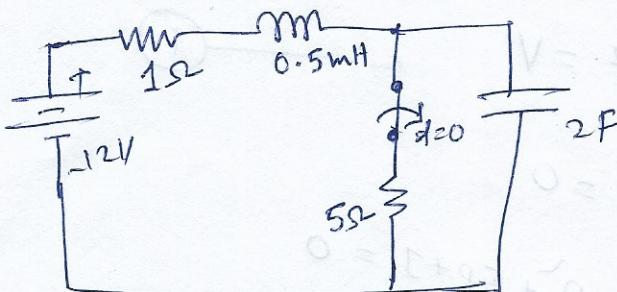

The switch in circuit of figure has been closed for a very long time. It opens at $t=0$, find

Ans:- At steady state (with switch is closed)
inductor behaves as a short circuit while
capacitor behaves as an open circuit.

$V_C(t)$ for $t > 0$ using differential equation approach.

$$i_L(0^-) = \frac{12}{1+5} = 2A, V_C(0^-) = 2 \times 5 = 10V.$$

at $t=0$, switch is open, then applying KVL

$$12 = 1 \cdot i(t) + 0.5 \frac{di(t)}{dt} + \frac{1}{2} \int_0^t i(t) dt + 10$$

$$\Rightarrow 2 = i(t) + 0.5 \frac{di(t)}{dt} + \frac{1}{2} \int_0^t i(t) dt$$

on differentiating we get

$$\Rightarrow 0 = \frac{di(t)}{dt} + 0.5 \frac{d^2i(t)}{dt^2} + \frac{1}{2} i(t)$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} + 2 \frac{di(t)}{dt} + i(t) = 0 \quad \Rightarrow p^2 + 2p + 1 = 0$$

$$p_{1,2} = -1$$

$$\Rightarrow i(t) = (K_1 + K_2 t) e^{-t}$$

$$\text{at } t=0^+ i(0^+) = i_L(0^-) = 2 = K_1 e^0 \Rightarrow K_1 = 2$$

$$V_C(0^+) = V_C(0^-) = 10 = \frac{1}{2} \int_0^{t=0} i(t) dt + 10 \Rightarrow K_2 = 2$$

$$i(t) = (2 + 2t) e^{-t}$$

$$V_C(t) = \frac{1}{2} \int_0^t i(t) dt + 10 = \int_0^t (1+t) e^{-t} dt + 10 = 12 - 2e^{-t} - te^{-t}$$